

MACOMTM

Partners in RF & Microwave



Introduction of Doherty Amplifiers

Xin Liu Shanghai WPC Team

Early days of Doherty Amplifier


MACOM



WILLIAM H. DOHERTY

Recipient, Morris Liebmann Memorial Prize, 1937

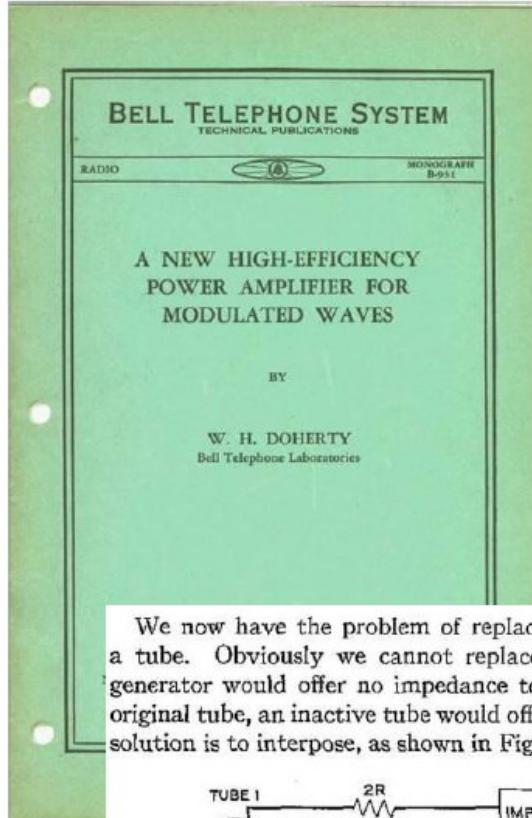Employed by Western Electric and
Bell Laboratories



We now have the problem of replacing this added generator with a tube. Obviously we cannot replace it directly, because while a generator would offer no impedance to the flow of current from the original tube, an inactive tube would offer an infinite impedance. The solution is to interpose, as shown in Fig. 3, a network having a certain


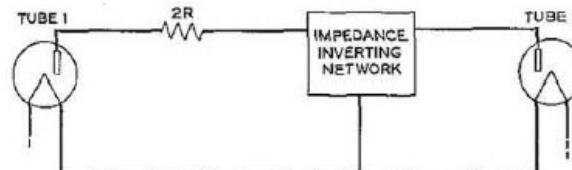
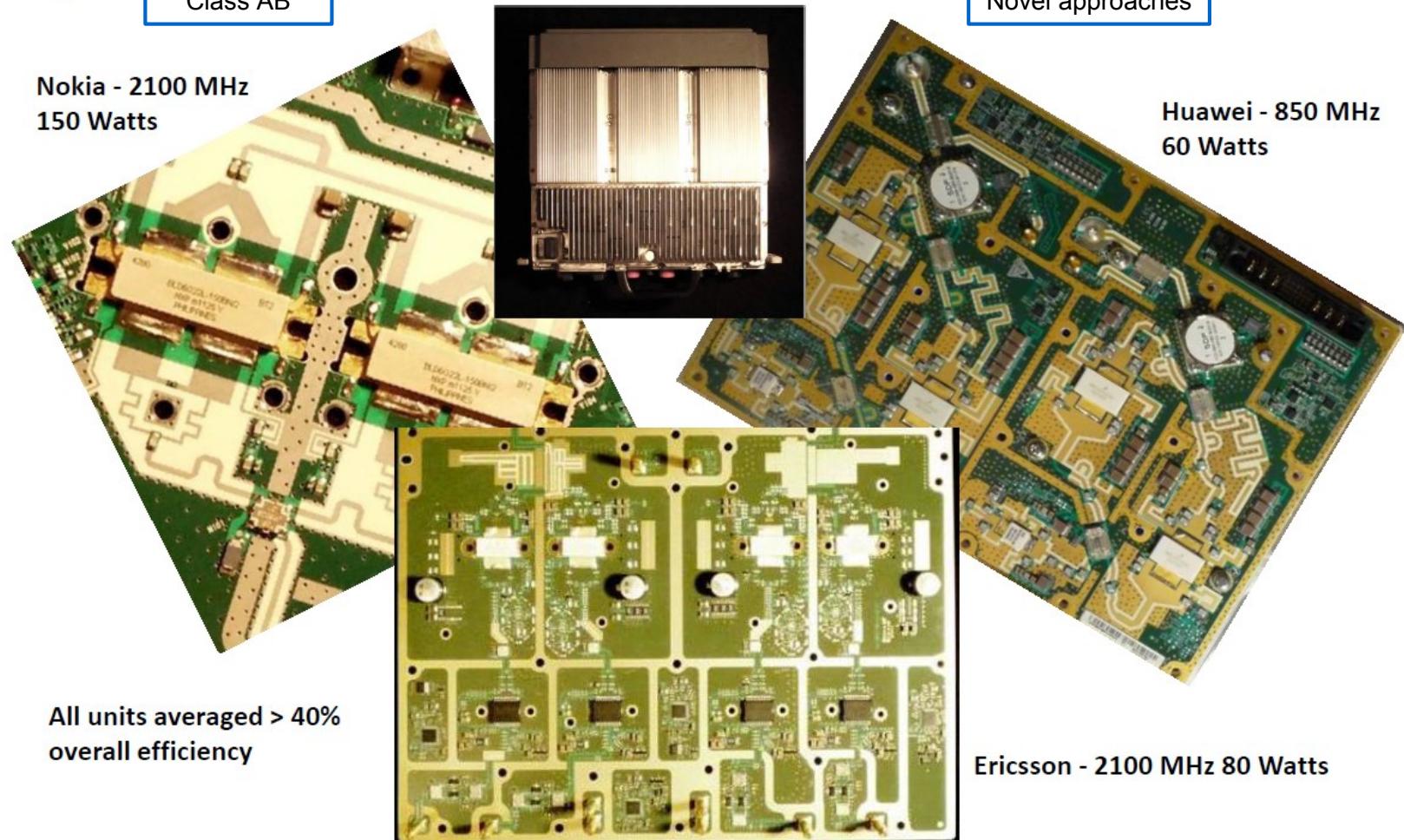


Fig. 3—Fundamental form of a high-efficiency circuit.



property, namely, that the impedance at the sending end is inversely proportional to the terminating impedance. This is a familiar property of quarter-wave transmission lines and their equivalent networks.

Doherty PA is Widely Used in Cellular Infrastructure Transmitter Now


MACOM

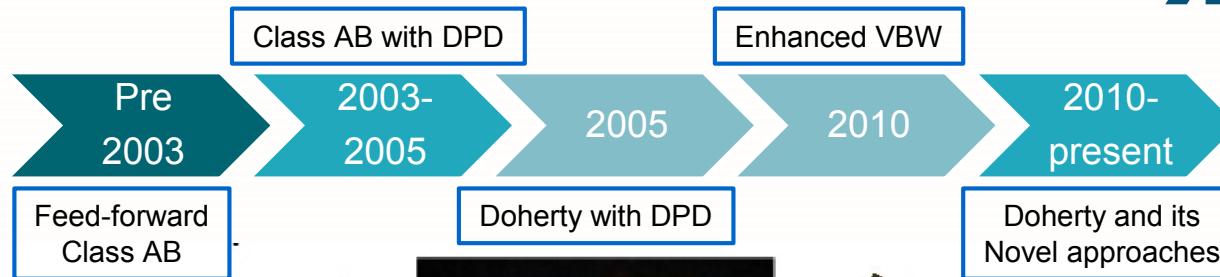

Doherty PA From Old Time to Now:

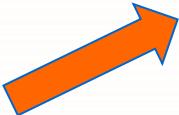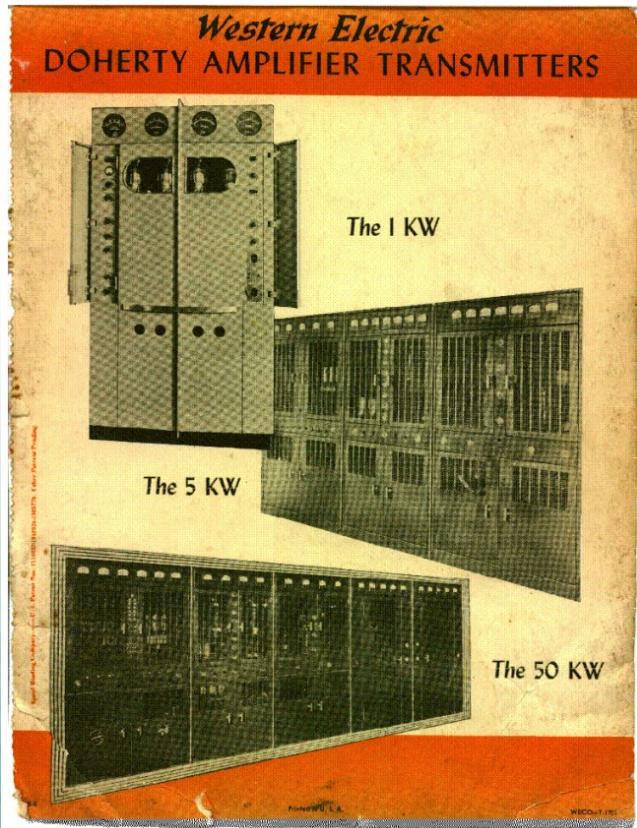

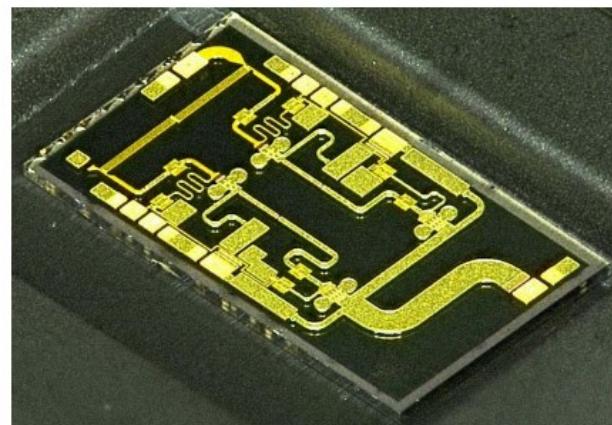2.14GHz N ways Doherty
4*25 W Cree HEMTs
Eff=61%@ Pout=20 W




mm Wave Doherty

A K-Band(22-24GHz) 5W Doherty Amplifier MMIC
Utilizing 0.15µm GaN on SiC HEMT Technology
Size: 3.4 mm x 2 mm

Basic Conceptions(1)

MACOM

For Ideal Class B Amplifier:

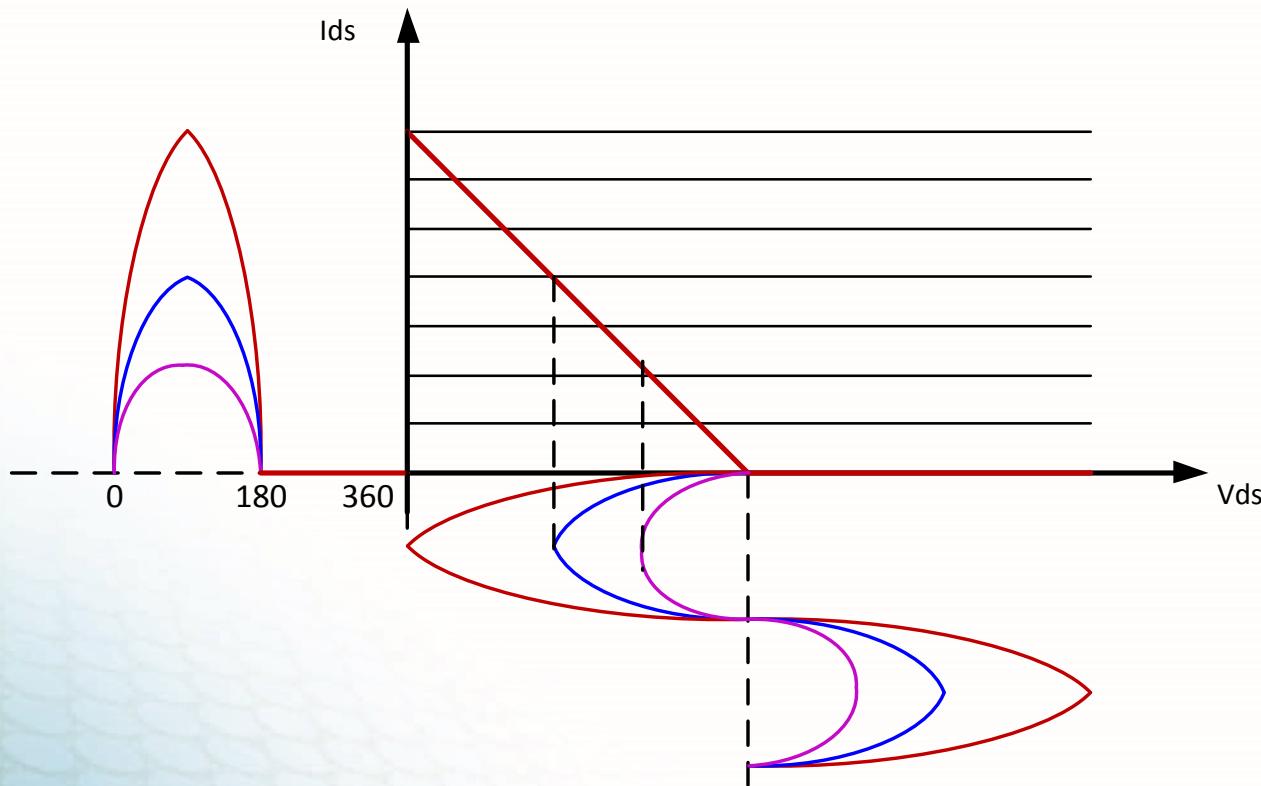


$$\eta = \frac{\pi}{4} \cdot \frac{V_{RF}}{V_{dd}}$$

MAX EFF only happens when MAX V_{RF} reaches;

Basic Conceptions(2)

MACOM

Two ways to Enhance Back Off Efficiency

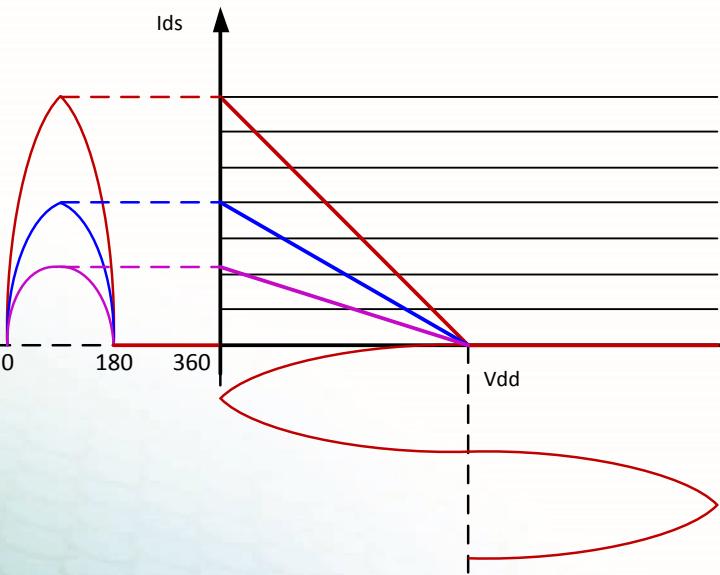


$$\eta = \frac{\pi}{4}$$

When V_{in} drops, V_{RF} still equal to V_{dd}
By Changing Z_{Load} , Which is also called: "Load Modulation"



W.H. Doherty Use This Way

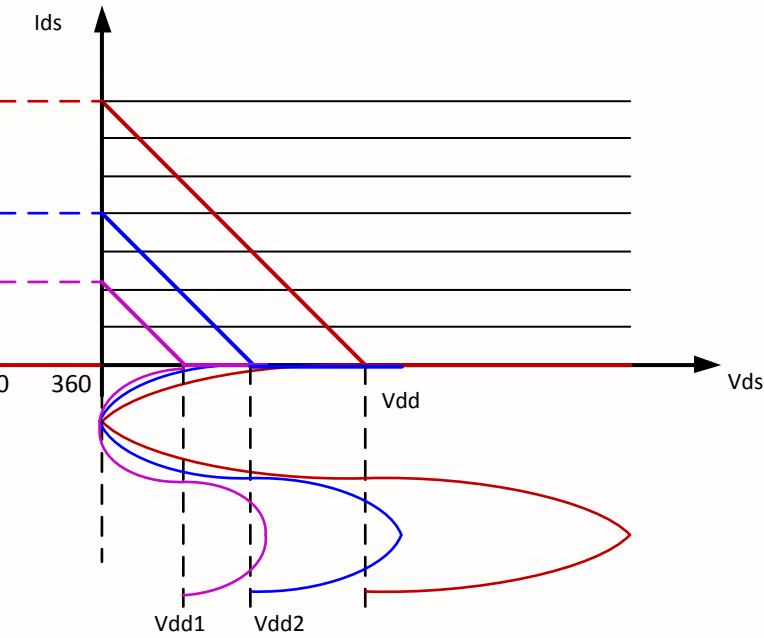

$$\eta = \frac{\pi}{4}$$



When V_{in} drops, V_{RF} still equal to MAX Voltage Swing
By Changing V_{dd}



E.T. Use This Way


Basic Conceptions(3)

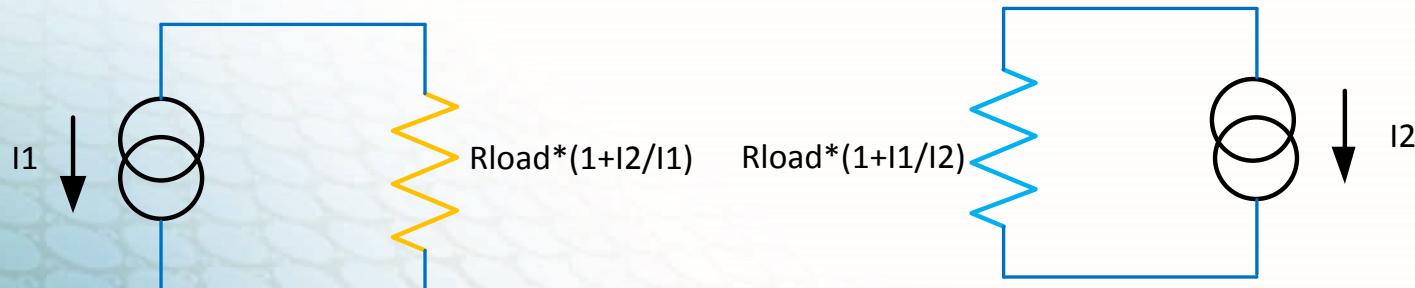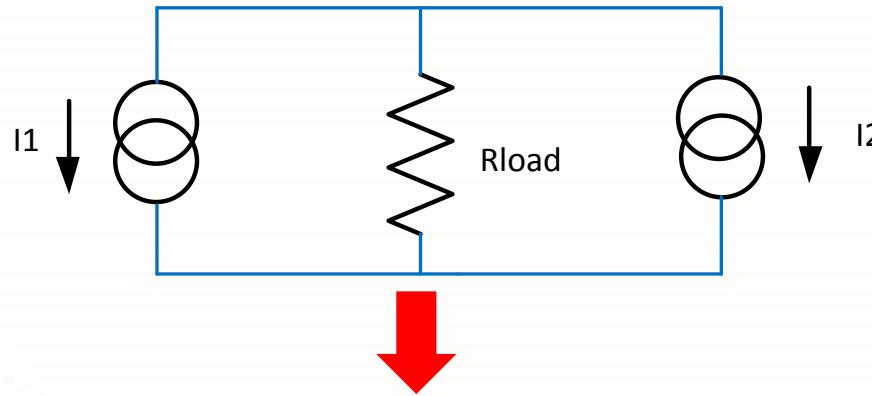W.H. Doherty had thought about Active Load Modulation:




Basic Conceptions(4)

MACOM

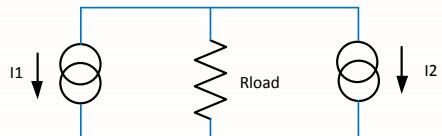

I₂: 0 → I₁

Load Modulation

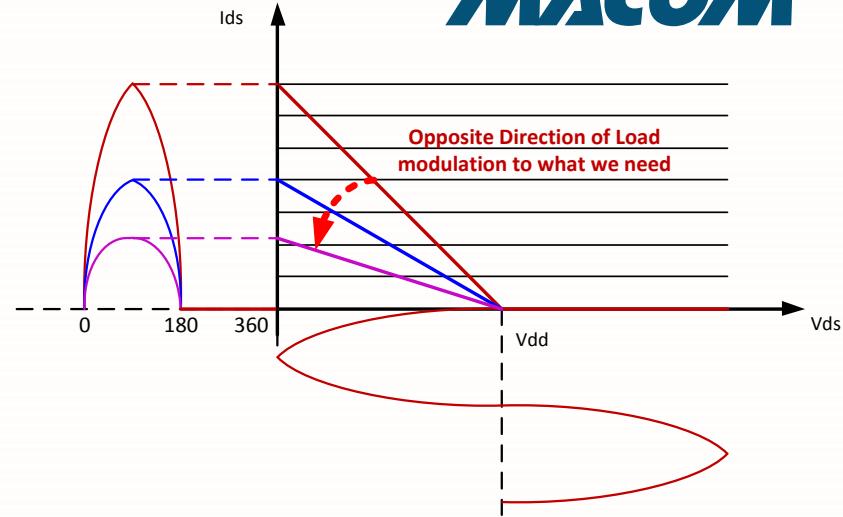


I₂: 0 → I₁, Z_{load} of Carrier: R_{load} → 2*R_{load}: Wrong Direction of Load Modulation!

Add Impedance Inverter



I₂: 0 → I₁

Load Modulation

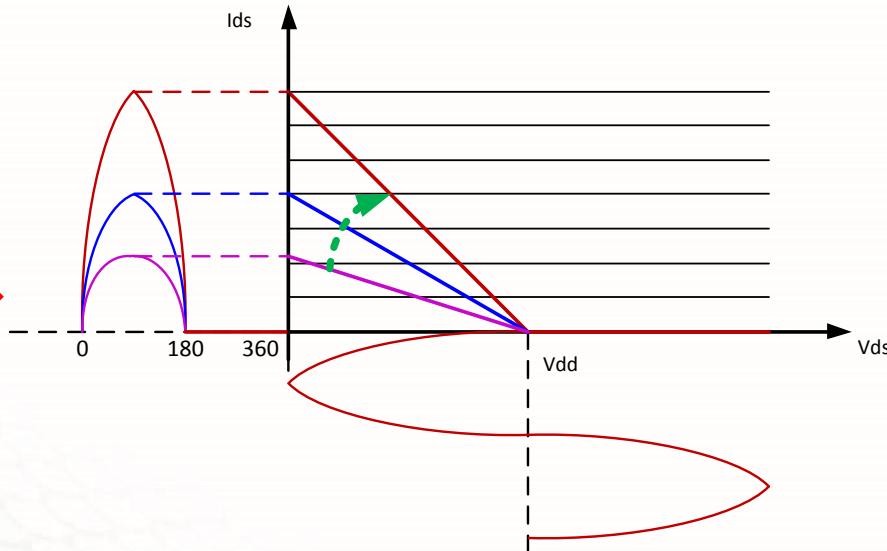


Impedance inverter makes load modulation into the correct direction:

I₂: 0 → I₁, Z_{Load} of Carrier : 2*R_{load} → R_{load}





A Real Doherty Circuit Diagram

MACOM

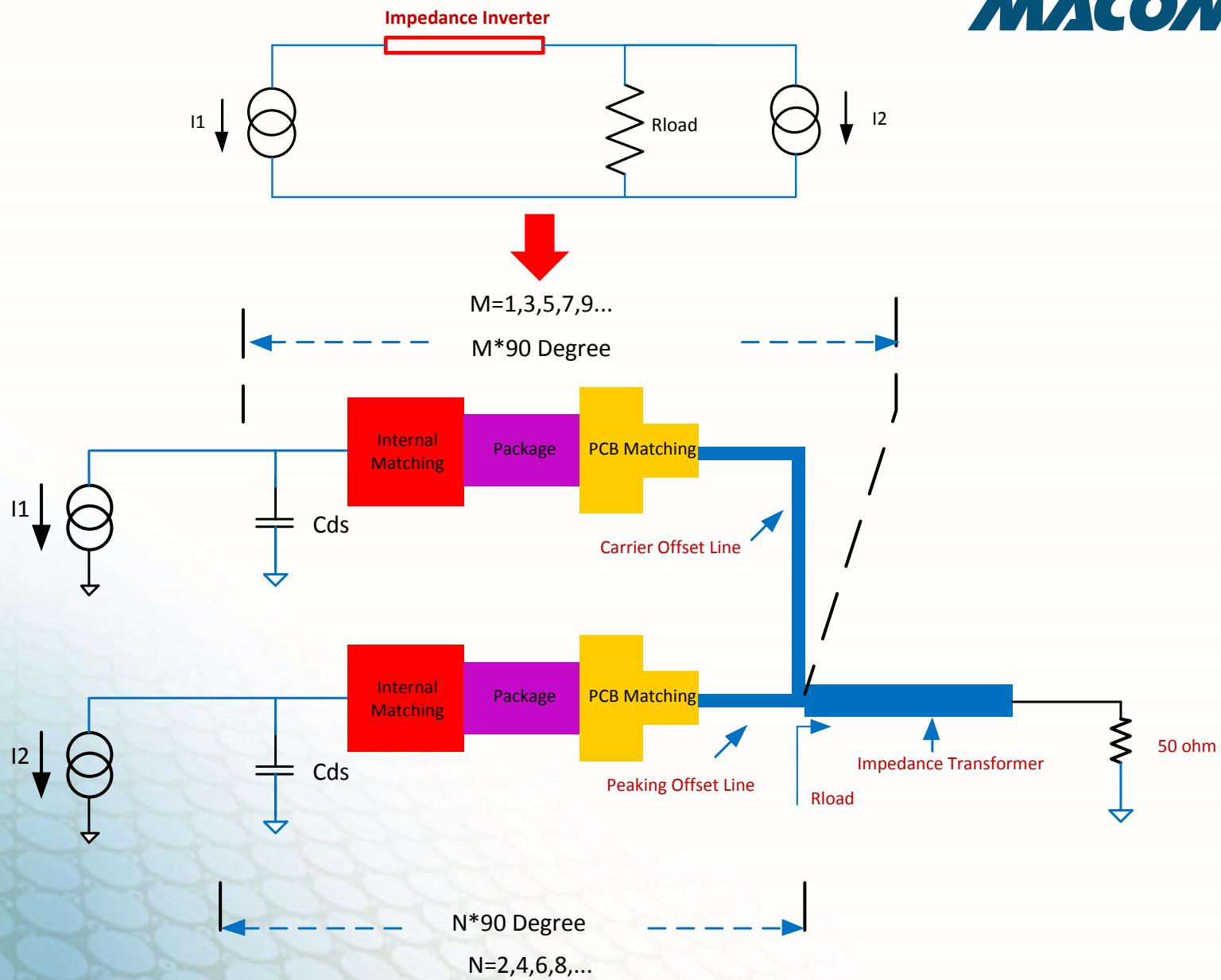

Behavior of An Ideal Symmetrical Doherty PA

MACOM

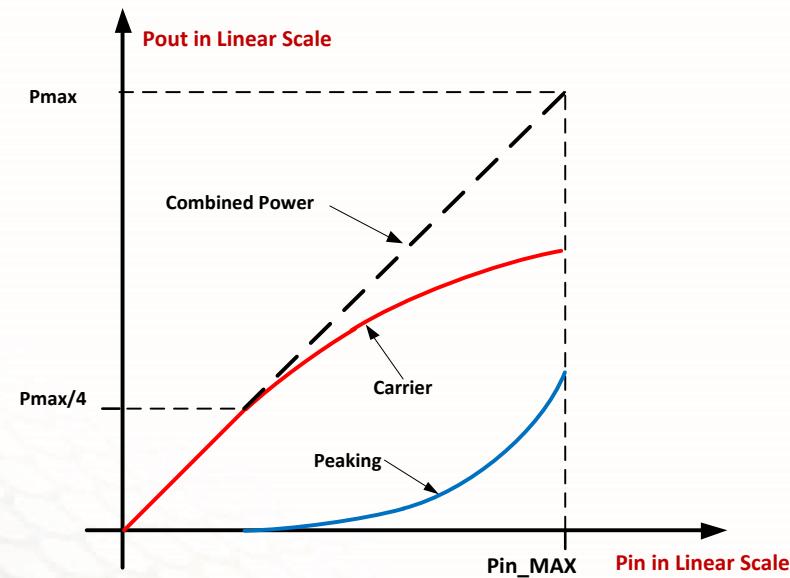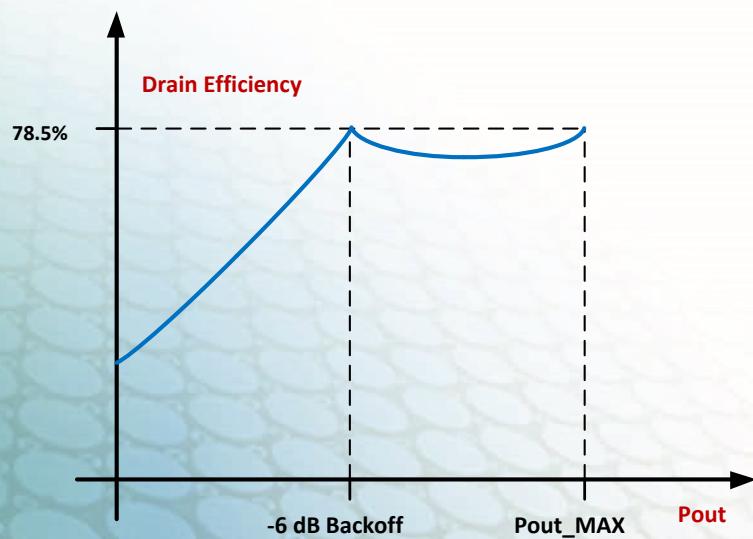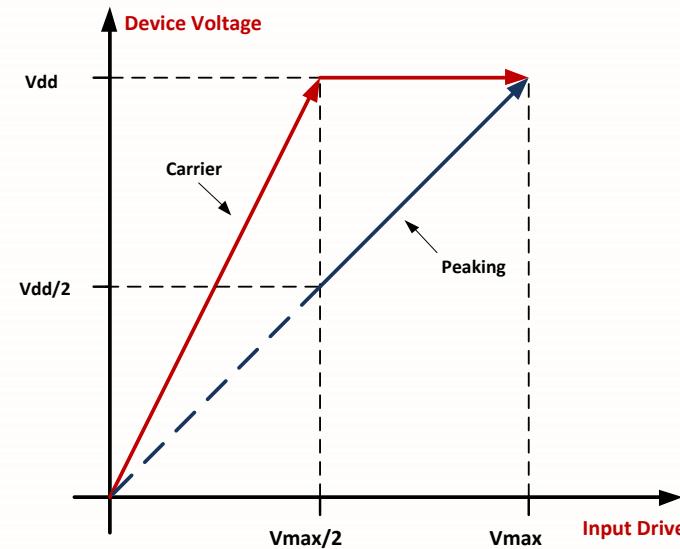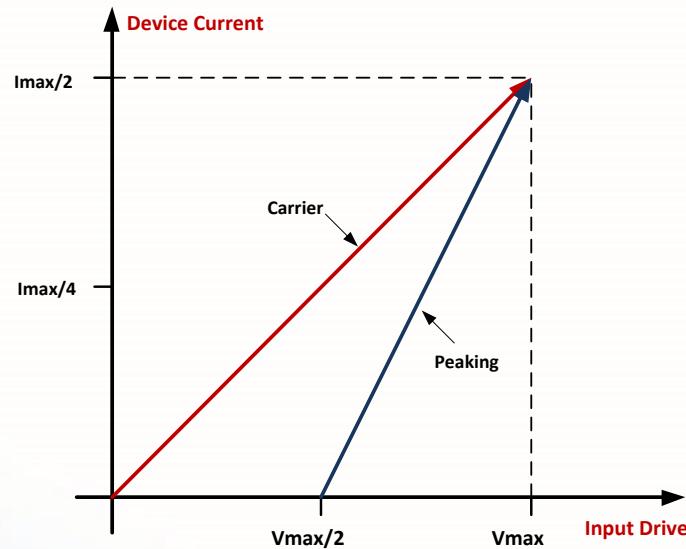

Some Key Parameters

MACOM

1. β : the ratio of peak fundamental current of Carrier and Peaking Amplifier

$$\beta = \frac{I_p}{I_c}$$

2. α : Normalize the input signal to be $0 < V_{in} < 1$,
and define the transition at which I_p starts to flow is $V_{in} = \alpha$

3. α & β have the relationship:

$$\alpha = \frac{1}{1 + \beta}; \beta = \frac{1 - \alpha}{\alpha}$$

4. α & β can determine Back Off point for MAX efficiency

$$Back_off(dB) = 20 \cdot \log(\alpha) = 20 \cdot \log\left(\frac{1}{1 + \beta}\right)$$

Doherty Parameters Calculation Flow:



Step1: Choose the required back off point for MAX efficiency: **Back_off(dB)**

Step2: Calculate α & β

$$\alpha = 10^{\frac{Back_off(dB)}{20}} \quad \beta = \frac{1 - \alpha}{\alpha}$$


Step3: Choose system reference value **Z0**

Step4: Calculate the load resistor value:

$$R = \alpha \cdot Z_0$$

Ex1: Symmetrical Doherty Calculation


MACOM

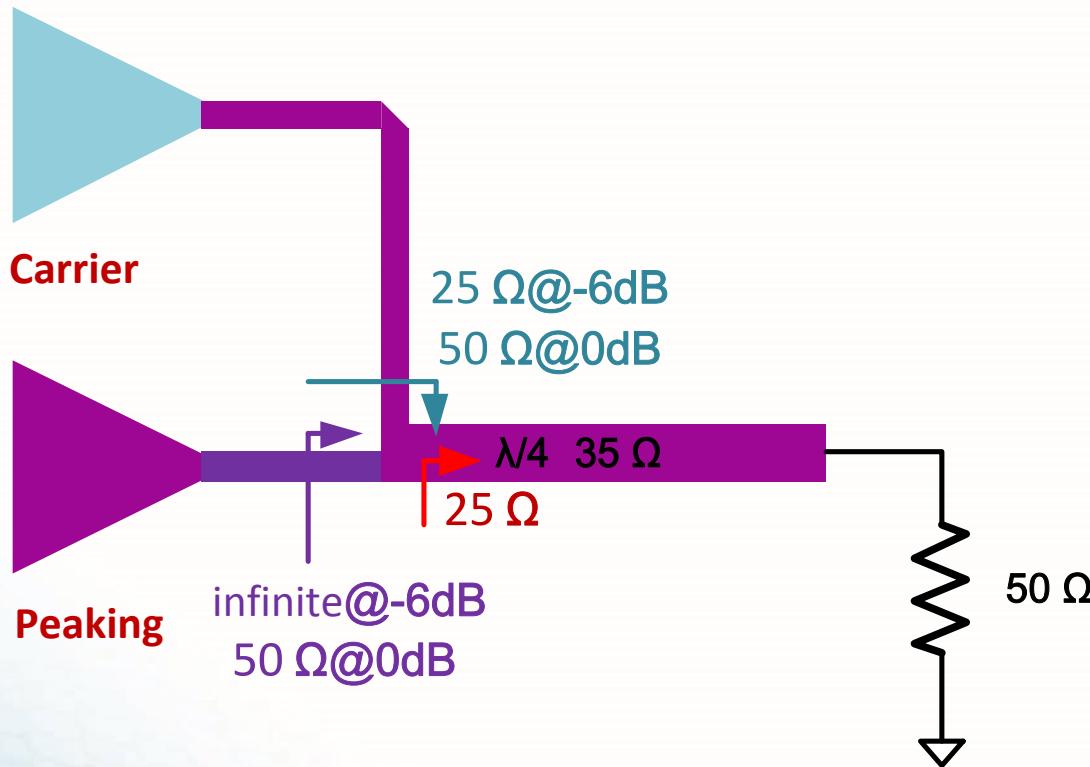

1. For Symmetrical Doherty, $I_c = I_p, \beta = 1$;
2. $\alpha = \frac{1}{1+\beta} = \frac{1}{2} = 0.5$, Back_{off(dB)} = $20 * \log(0.5) = -6 \text{ dB}$
3. Choose $Z_0=50 \text{ ohm}$ as the system reference impedance
4. $R = \alpha \cdot Z_0 = 0.5 * 50 \text{ ohm} = 25 \text{ ohm}$

EX2: Asymmetrical Doherty Calculation(1)


MACOM

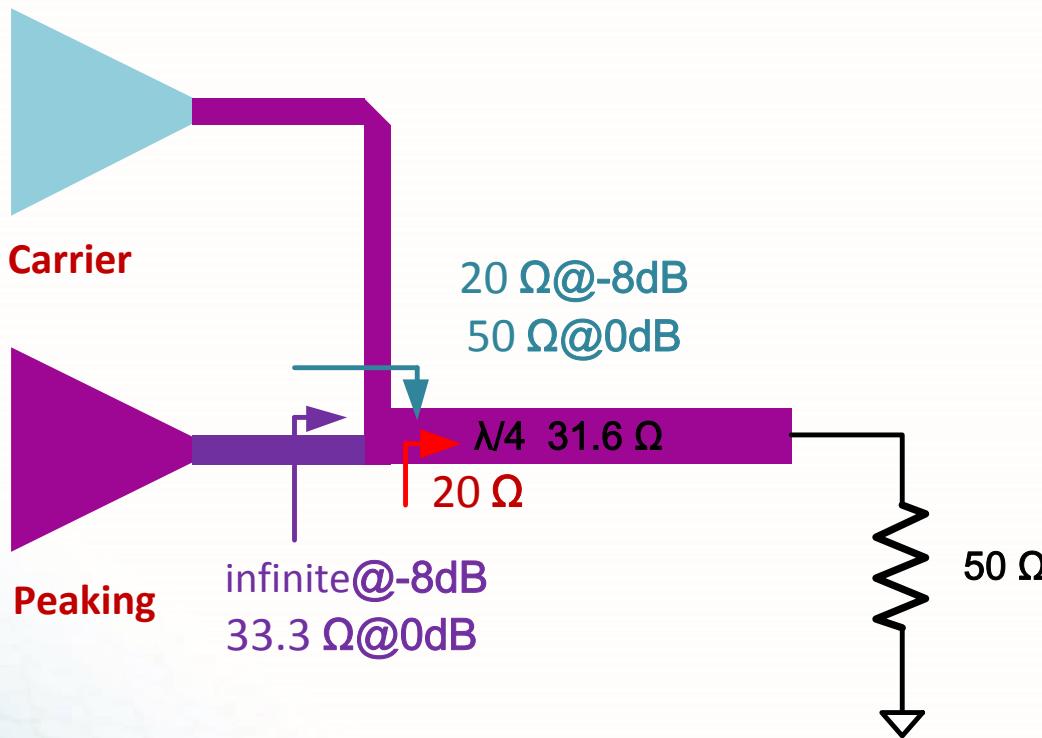

1. For Asymmetrical Doherty, $I_p = 1.5 * I_c, \beta = 1.5$;
2. $\alpha = \frac{1}{1+\beta} = \frac{1}{2.5} = 0.4$, Back_{off(dB)} = $20 * \log(0.4) = -7.96 \text{ dB}$
3. Choose $Z_0 = 50 \text{ ohm}$ as the system reference impedance
4. $R = \alpha \cdot Z_0 = 0.4 * 50 \text{ ohm} = 20 \text{ ohm}$

EX3: Asymmetrical Doherty Calculation(2)

MACOM

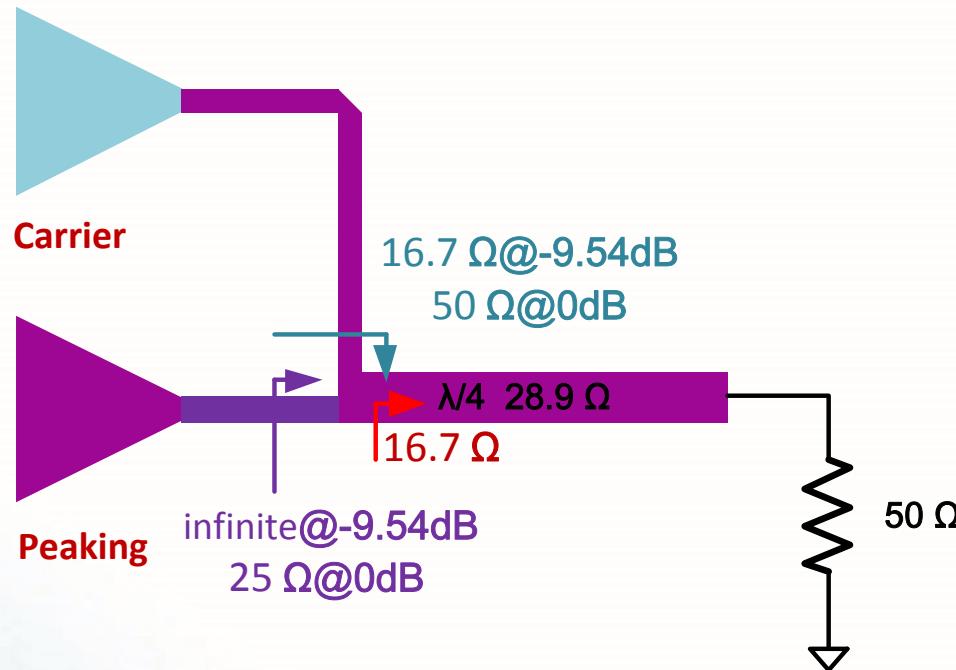


1. For Asymmetrical Doherty, $I_p=2*I_c, \beta=2$;
2. $\alpha = \frac{1}{1+\beta} = \frac{1}{3} = 0.33$, Back_{off(dB)} = $20 * \log(0.33) = -9.54\text{dB}$
3. Choose $Z_0=50 \text{ ohm}$ as the system reference impedance
4. $R = \alpha \cdot Z_0 = 0.33 \cdot 50 \text{ ohm} = 16.7 \text{ ohm}$

Doherty Design Example


A 1.8GHz 60W Asymmetrical Doherty Amplifier Design

Step1: Doherty Topology Selection

MACOM

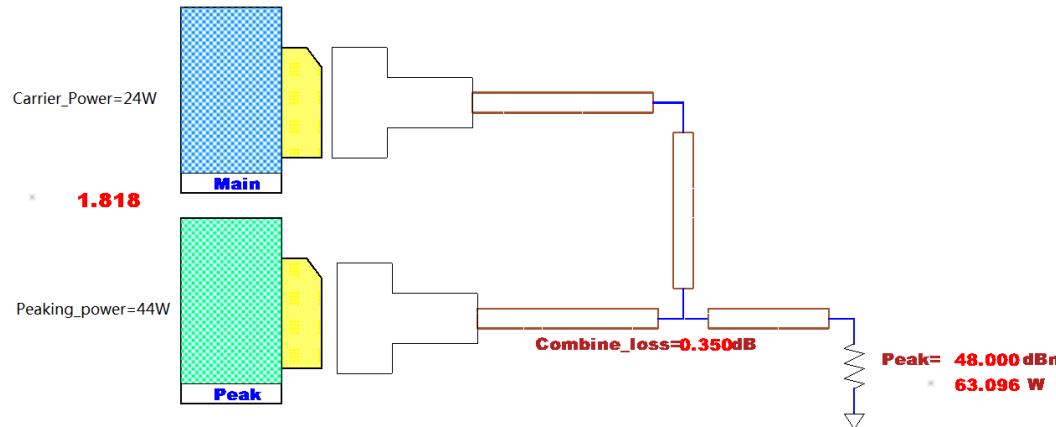

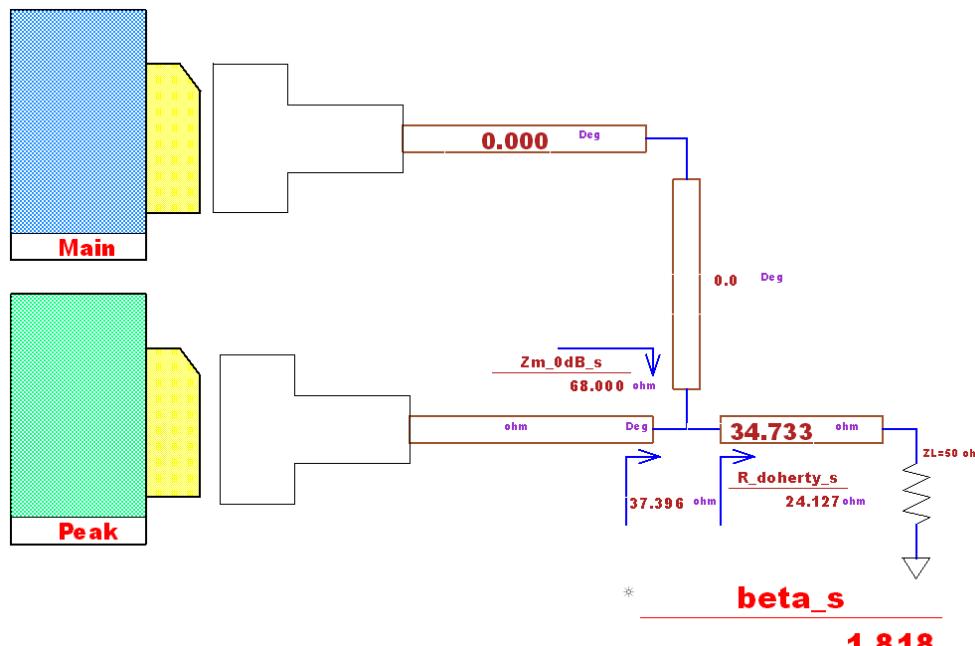Ppeak= 48 dBm;
Pav= 39dBm
9 dB Back_Off Design;




Z0=68 ohm;

Doherty Design Example

A 1.8GHz 60W Asymmetrical Doherty Amplifier Design

Step2: Impedance Selection for Carrier Side

MACOM

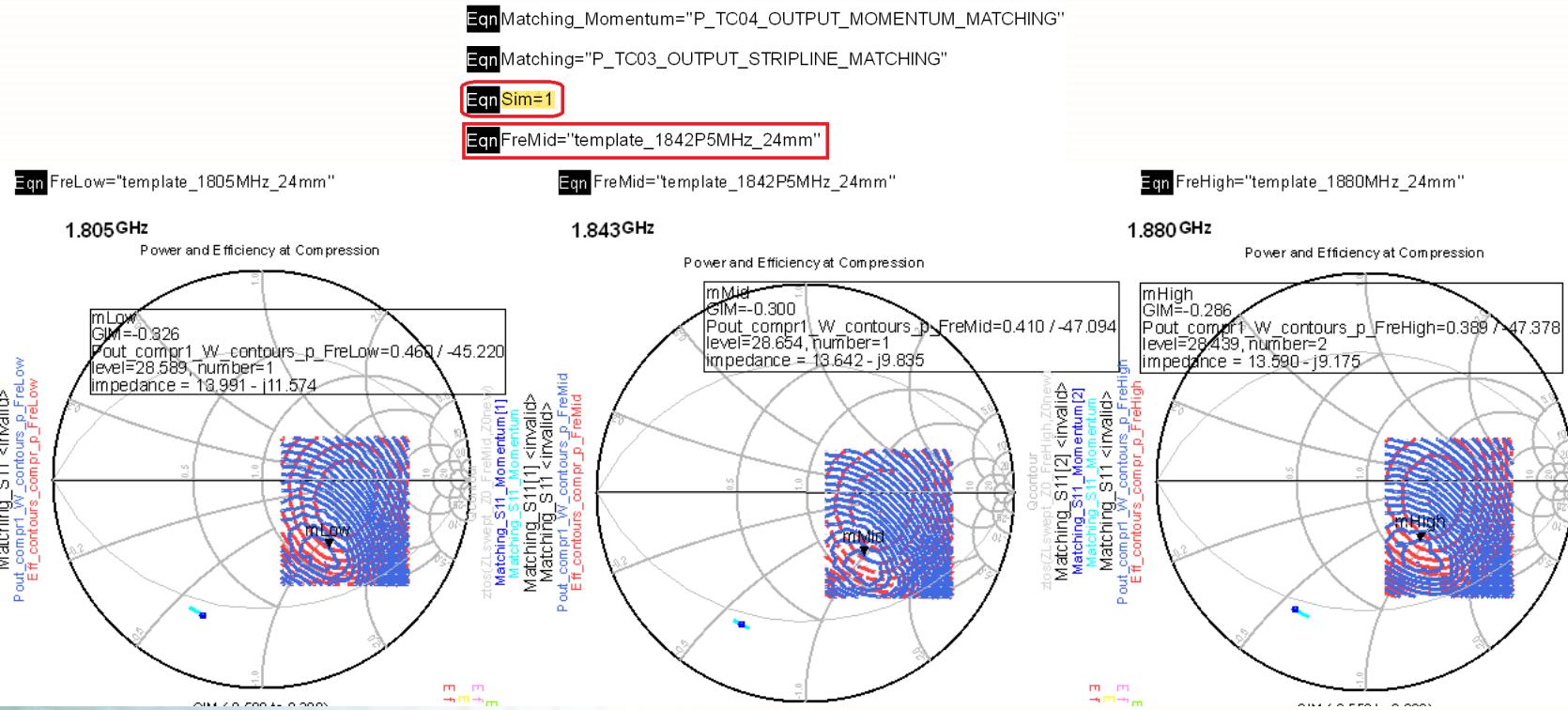

Backoff point	1.805GHz	1.843GHz	1.880GHz
Pout	44.69dBm	44.52dBm	44.59dBm
Pout	29.44W	28.34W	28.77W
Eff	62.78%	64.94%	64.37%
Gain	19.39dB	19.82dB	19.43dB

Doherty Design Example

A 1.8GHz 60W Asymmetrical Doherty Amplifier Design


Step3: PCB Matching for Carrier Amplifier

MACOM






Var	Eqn	VAR
Source_Load2		
Z_low=13.991+j*11.574		
Z_mid=13.642+j*9.835		
Z_high=13.59+j*9.175		
freq	Zmatch_lead	
1.80 GHz	14.56 -j10.57	
1.84 GHz	13.89 -j10.06	
1.88 GHz	13.28 -j9.54	

MSub

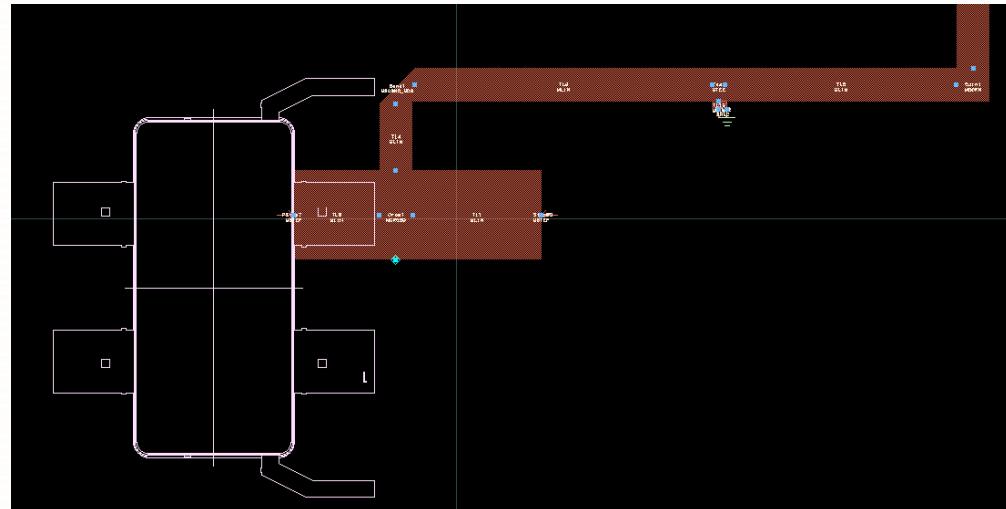MSUB
MSub1
H=30 mil
Er=3.66
Mur=1
Cond=57.15E6
Hu=3.9e+34 mm
T=35 um
TanD=0.0031
Rough=0.00 mm
Bbase=
Dpeaks=



Power and Efficiency at Compression

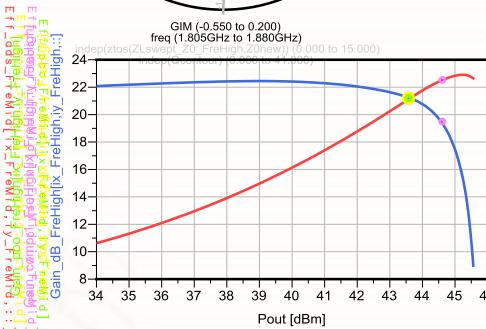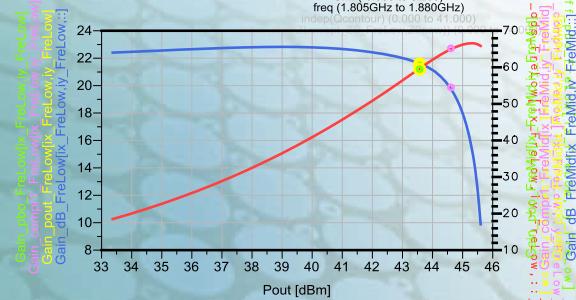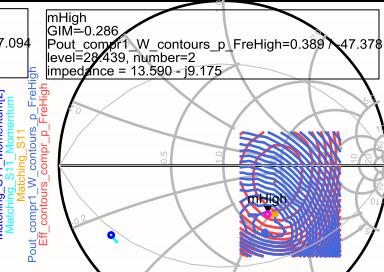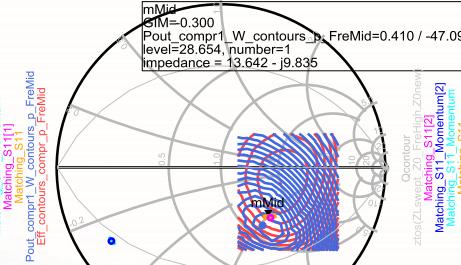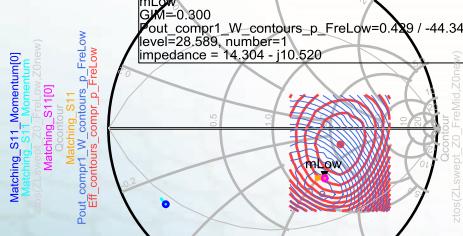


Doherty Design Example


A 1.8GHz 60W Asymmetrical Doherty Amplifier Design

Step4: High Load Performance Checking

MACOM

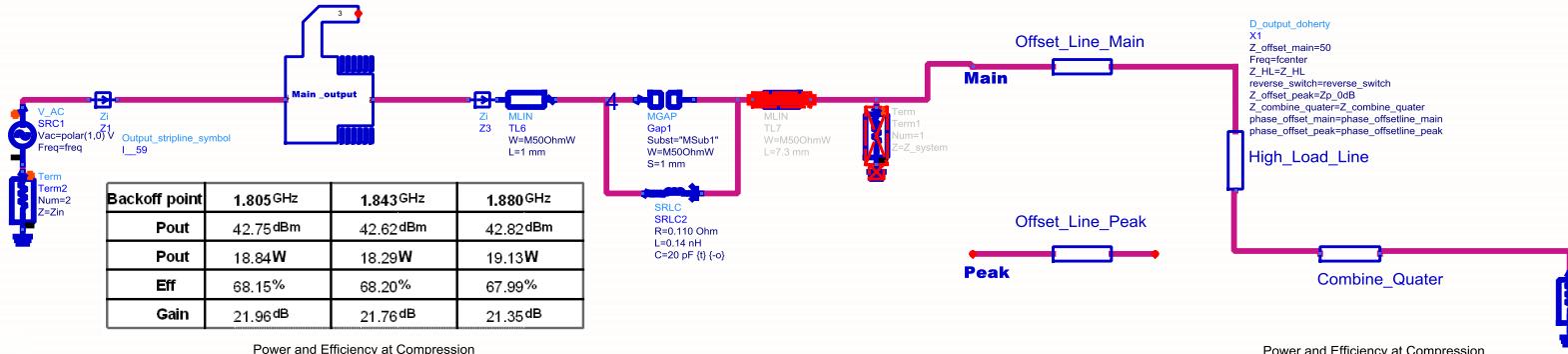

Power and Efficiency at Compression

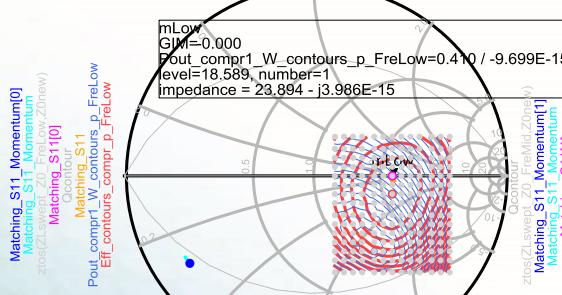

GIM (-0.500 to 0.200)
freq (1.805GHz to 1.880GHz)
indep(Qcontour) (0.000 to 41.000)


Gain_100_phi_FrelHigh, FrelLow, FrelHigh
Gain_compr_FrelLow, FrelLow, FrelHigh
Gain_db_FrelLow, FrelLow, FrelHigh
Gain_db_FrelHigh, FrelHigh, FrelLow

Pout [dBm]

[: wGain_phi_FrelHigh, FrelLow, FrelHigh]
[: wGain_compr_FrelLow, FrelLow, FrelHigh]
[: wGain_db_FrelLow, FrelLow, FrelHigh]
[: wGain_db_FrelHigh, FrelHigh, FrelLow]


Gain_100_phi_FrelHigh, FrelLow, FrelHigh
Gain_compr_FrelLow, FrelLow, FrelHigh
Gain_db_FrelLow, FrelLow, FrelHigh
Gain_db_FrelHigh, FrelHigh, FrelLow

Power and Efficiency at Compression

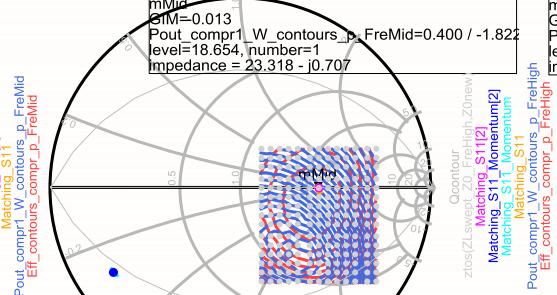

indep(ztos(Zswept_20_FrelHigh_Z0new)) (0.000 to 41.000)
indep(Qcontour) (0.000 to 41.000)

Power and Efficiency at Compression

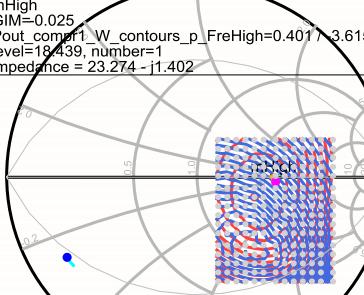

indep(ztos(Zswept_20_FrelHigh_Z0new)) (0.000 to 15.000)
indep(Pout_compr1_W_contours_p_FrelHigh) (0.000 to 41.000)




Eff_phi_FrelHigh, FrelLow, FrelHigh
Eff_compr_FrelLow, FrelLow, FrelHigh
Eff_db_FrelLow, FrelLow, FrelHigh
Eff_db_FrelHigh, FrelHigh, FrelLow

Doherty Design Example

A 1.8GHz 60W Asymmetrical Doherty Amplifier Design

Step5: HB Simulation for Carrier Amplifier

MACOM

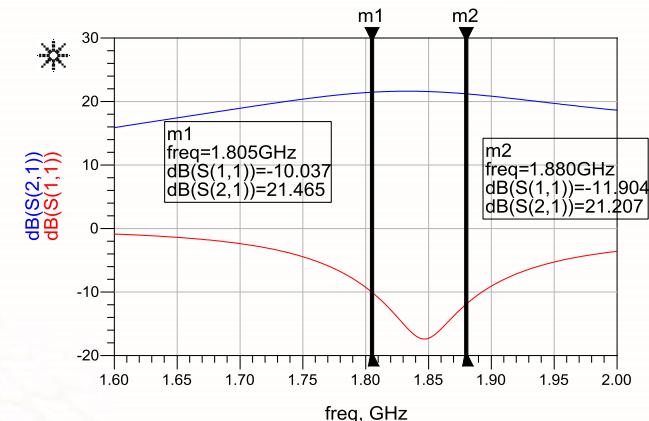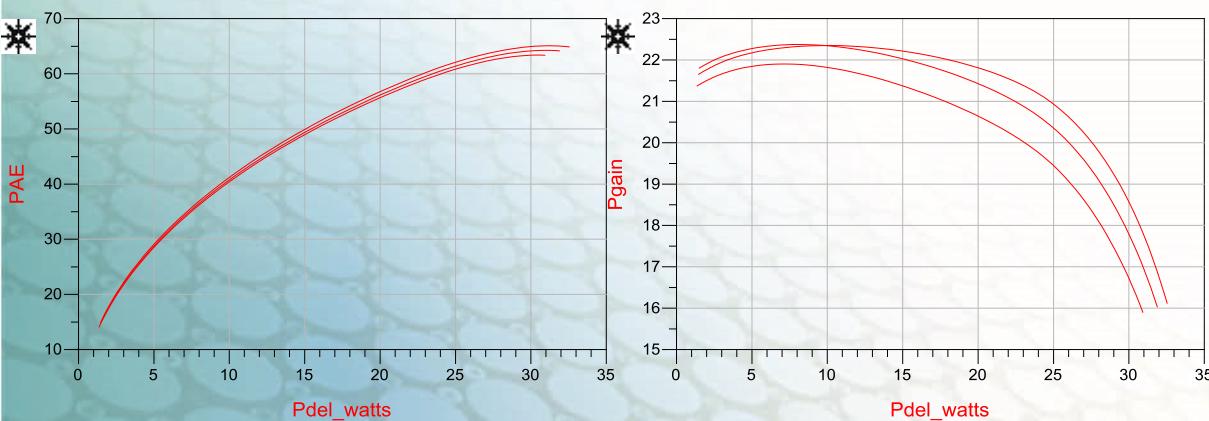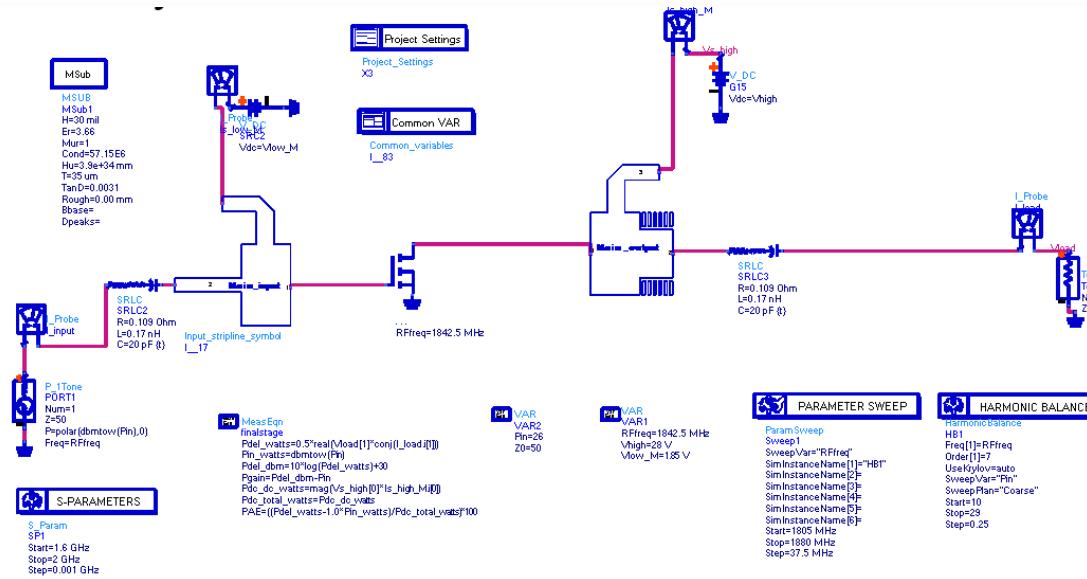


Doherty Design Example

A 1.8GHz 60W Asymmetrical Doherty Amplifier Design




Step6: PCB Matching Design for Peaking Amplifier

MACOM

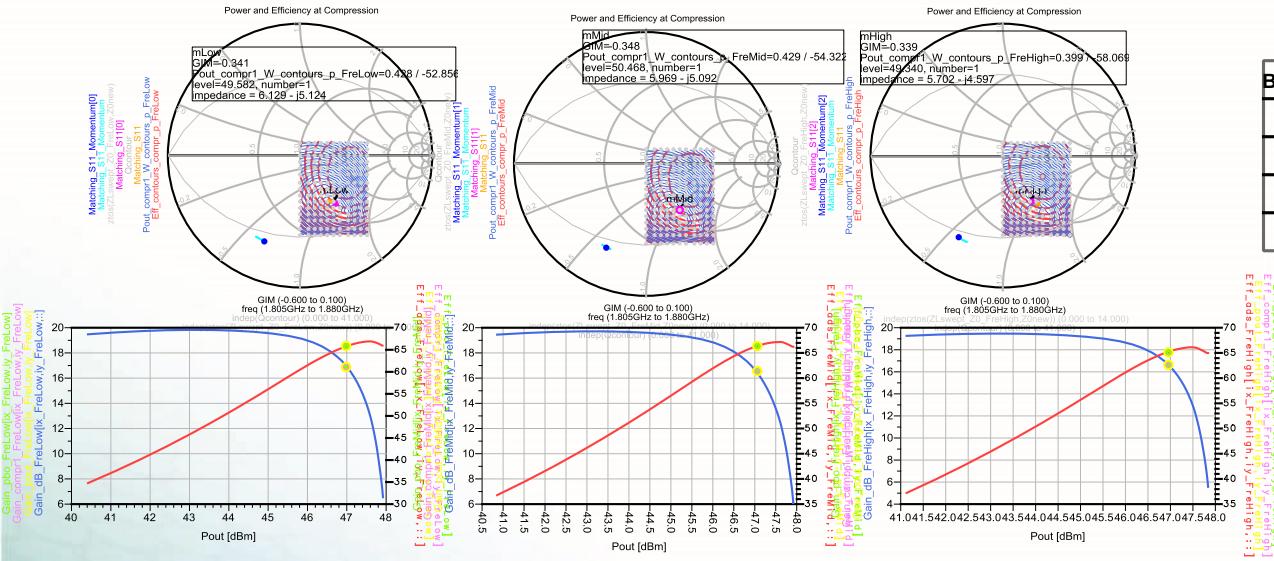

Backoff point	1.805GHz	1.843GHz	1.880GHz
Pout	46.99dBm	47.04dBm	46.98dBm
Pout	50.03W	50.54W	49.85W
Eff	65.80%	66.32%	65.29%
Gain	16.95dB	16.52dB	16.55dB

Active model simulated Class C results


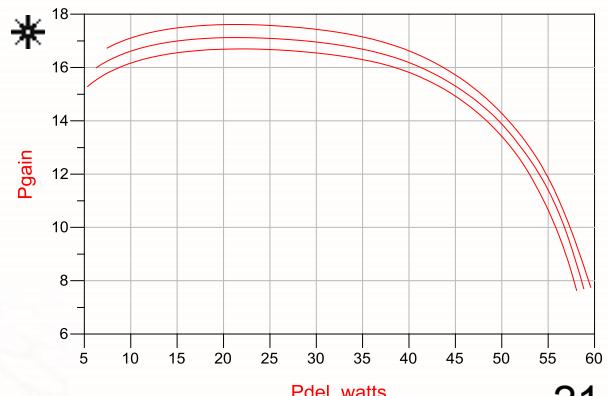
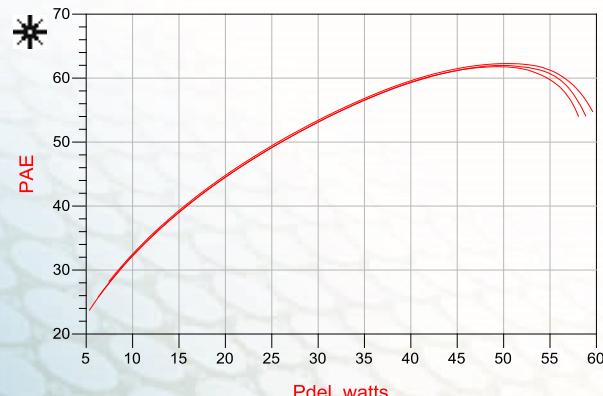
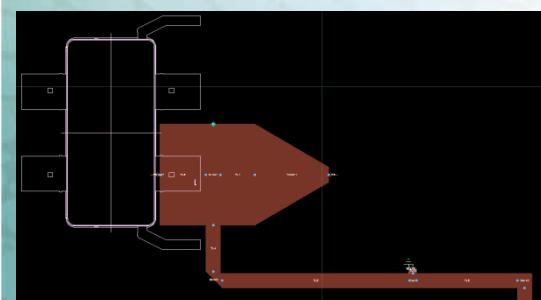


Doherty Design Example

A 1.8GHz 60W Asymmetrical Doherty Amplifier Design

MACOM

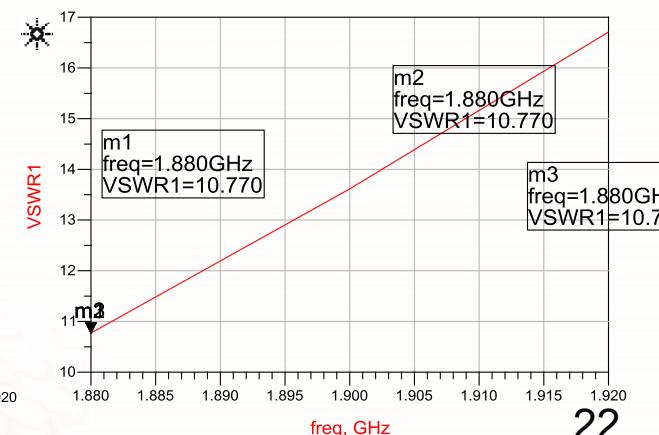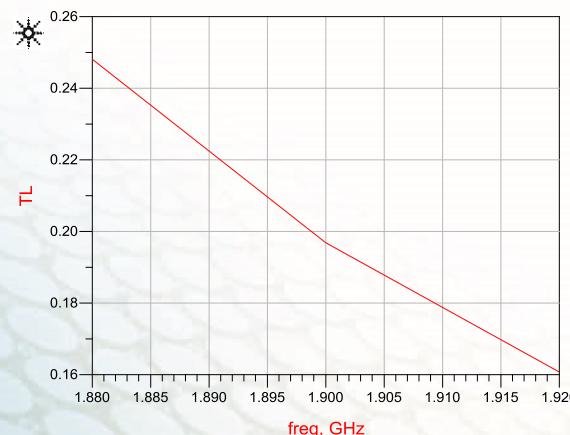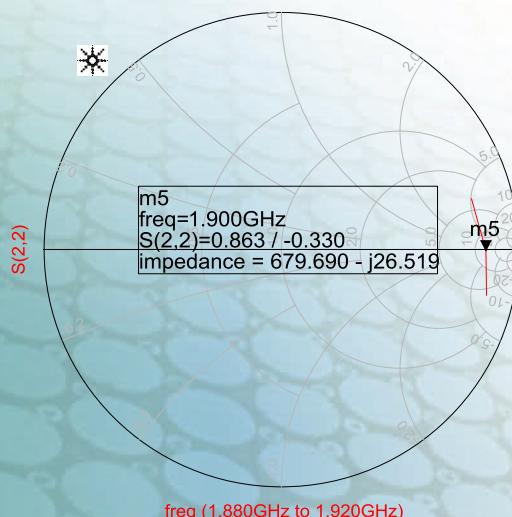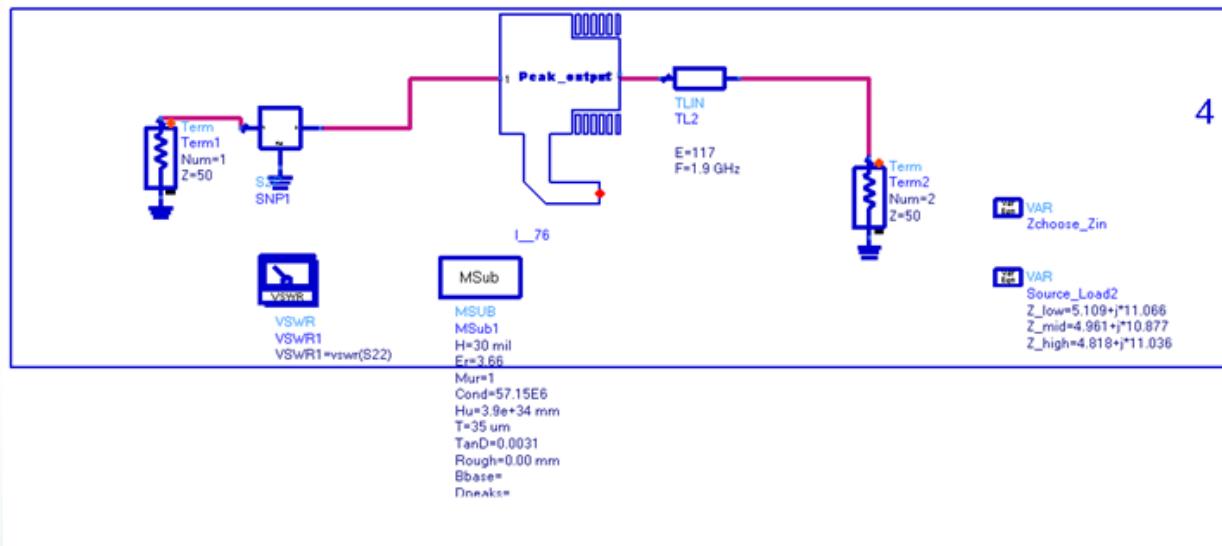Step7: Calculation the Length of Off State Offset Line for Peaking Amplifier
 (Base on Off State S parameter of Peaking Transistor)






Doherty Design Example

MACOM

A 1.8GHz 60W Asymmetrical Doherty Amplifier Design

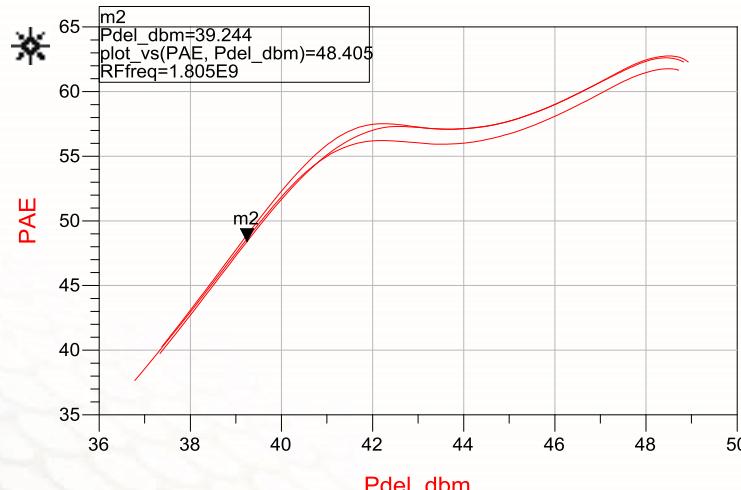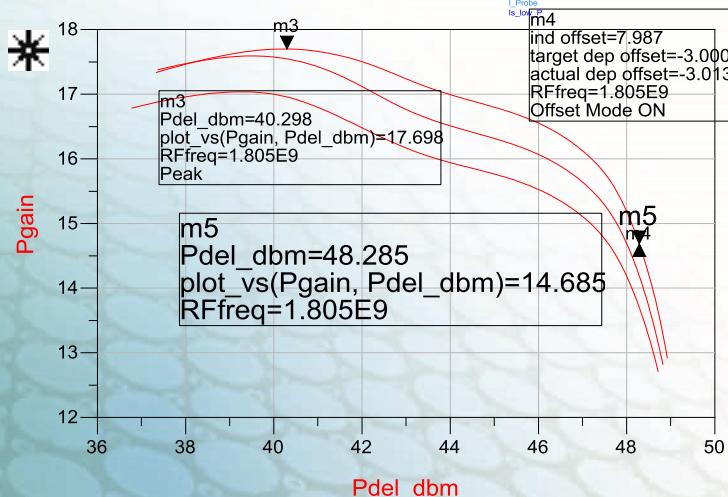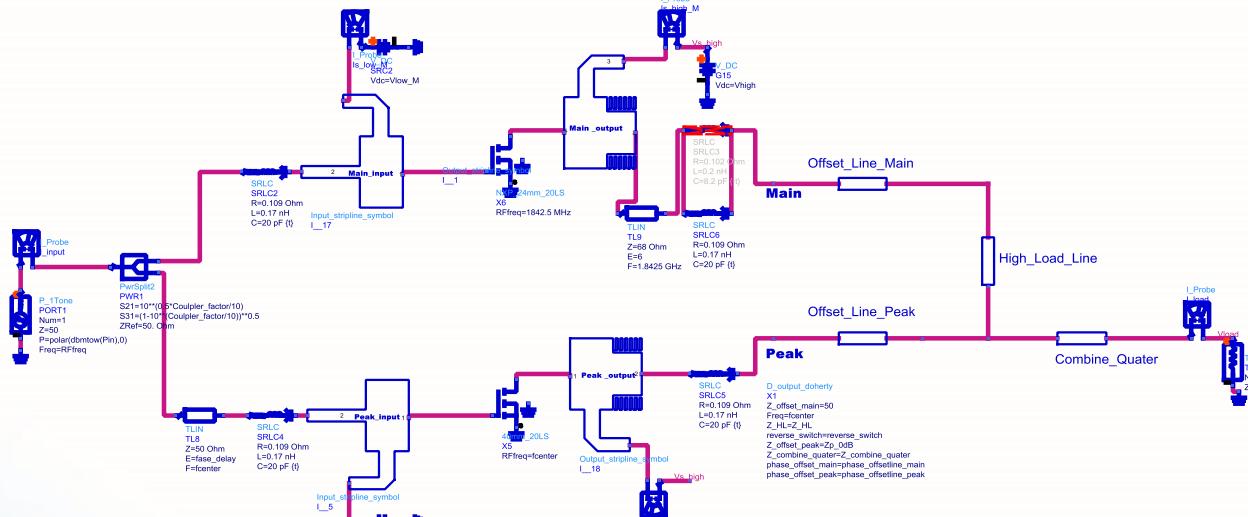Step8: Fine Tuning of Whole Doherty Based on HB Simulation




Ppeak=48.3 dBm, EFF=48%@ 9dB Back off

Doherty Design Example

A 1.8GHz 60W Asymmetrical Doherty Amplifier Design

Step9: Final PCB Layout

MACOM

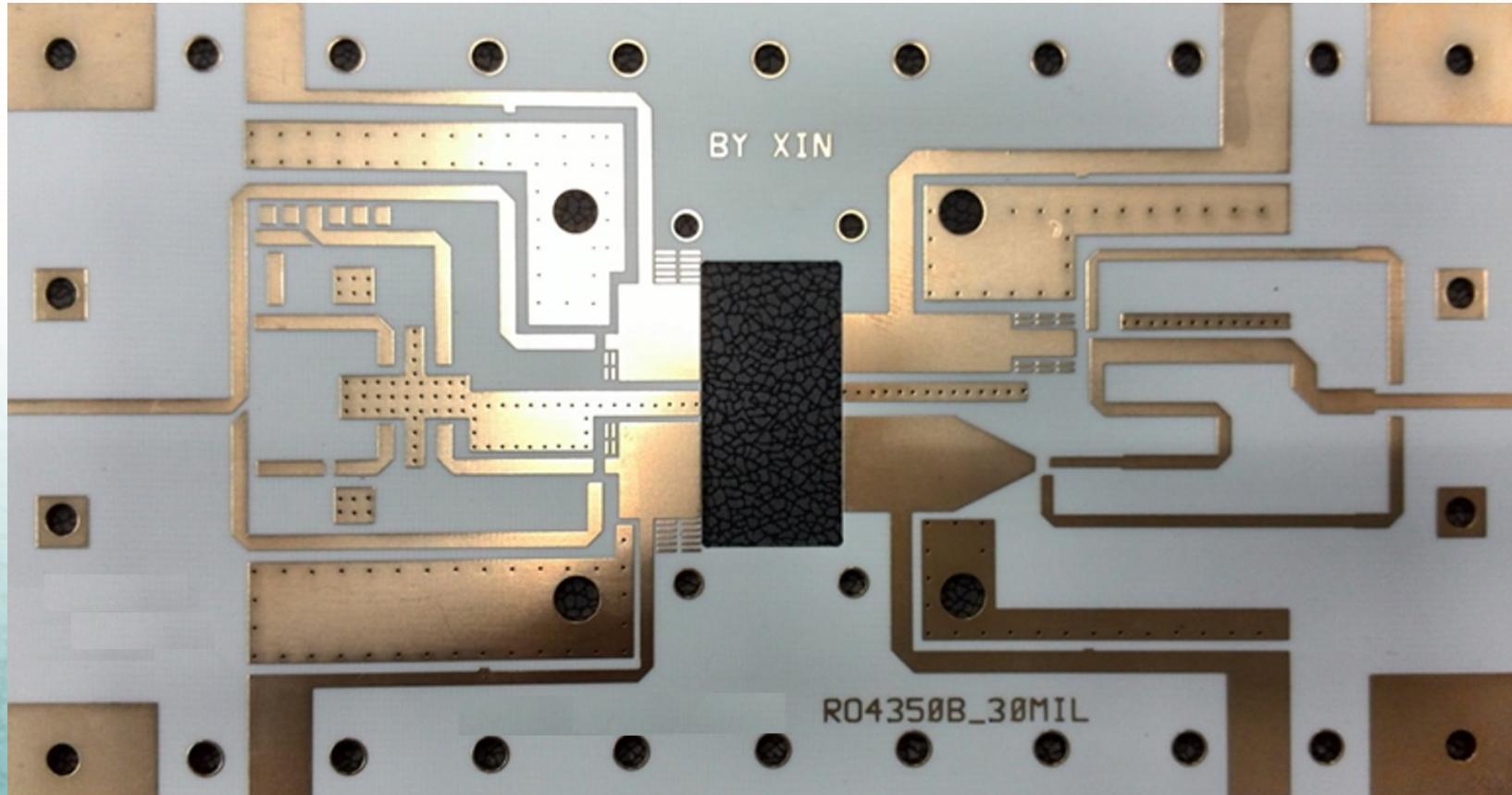



**Any Questions?
Thanks**



Reference:

- [1] Cripps, S., “Doherty RF Power Amplifiers, Theory and Practice”,
Short Course SC-4, 2009 International Microwave Symposium, Boston, June 2009
- [2] Cripps, S., *RF Power Amplifiers for Wireless Communications*, Artech House, 1999, p 225-235
- [3] Son, J., Kim, I., Mon, J., Lee, J., Kim, B., “A Highly Efficiency Asymmetric Doherty Power Amplifier with a New Output Combining Circuit,” *2011 IEEE COMCAS*, Tel Aviv, November 2011.
- [4] Charles F. Campbell, Kim Tran, Ming-Yih Kao and Sabyasachi Nayak, “K-Band 5W Doherty Amplifier Using 0.15um GaN on SiC HEMT Technology”.