

**MACOM**<sup>TM</sup>

*Partners in RF & Microwave*



## Taking A Closer Look At Doherty Amplifiers

Xin Liu Shanghai WPC Team


Dec. 2015

## Contents:

- Bandwidth analysis of Doherty amplifier
- Advanced Doherty topologies introduction
- Doherty analysis tools introduction




# Center Frequency Analysis of Ideal Doherty PA

**MACOM**

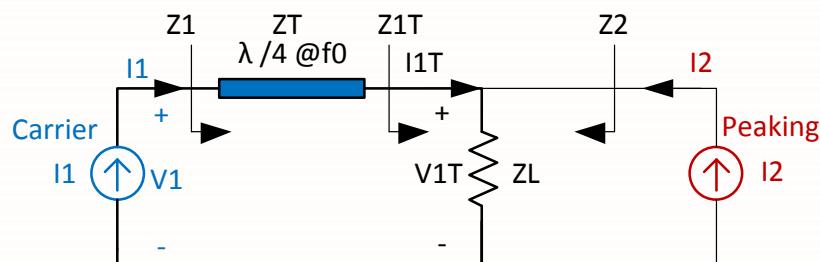


$$I_1 = \xi \cdot \frac{I_{max1}}{2}$$
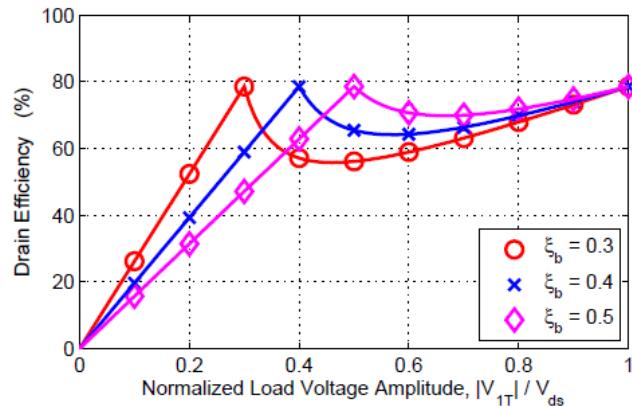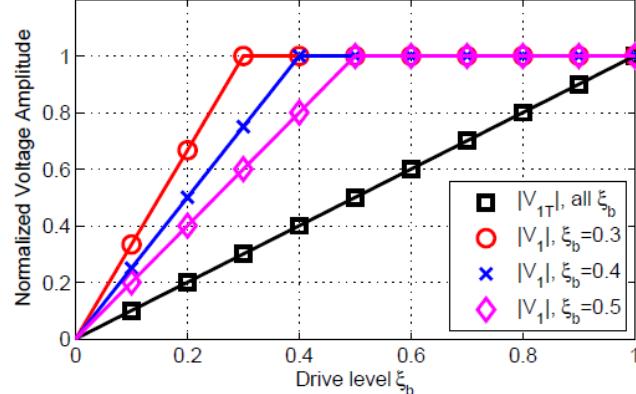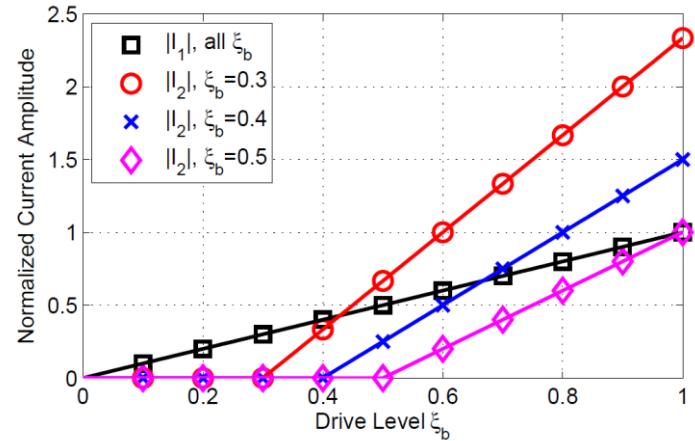
$$I_2 = \begin{cases} 0, & 0 < \xi < \xi_b \\ \frac{I_{max1}}{2} \cdot \frac{\xi - \xi_b}{\xi_b} \cdot e^{-j\theta}, & \xi_b < \xi < 1 \end{cases}$$



(a)

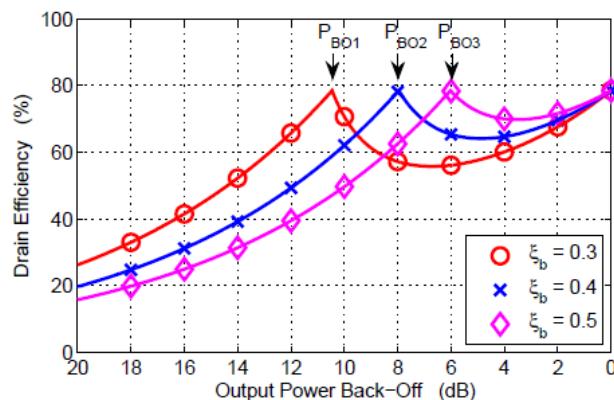


(b)

Company Confidential, Internal Use Only

# Frequency Response of Ideal Doherty PA(1)



**MACOM**

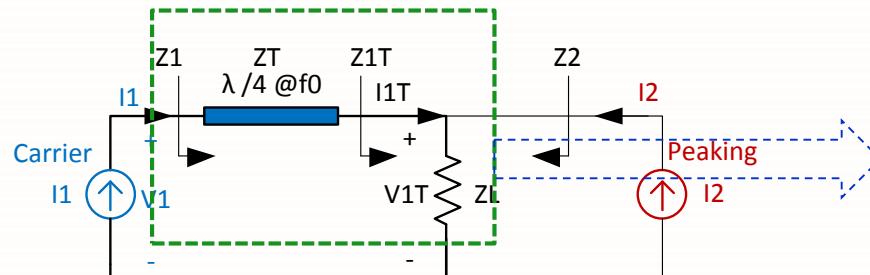

$$Z = \begin{bmatrix} Z_T \cdot \frac{Z_L \cdot \cos(\theta) + j \cdot Z_T \cdot \sin(\theta)}{Z_T \cdot \cos(\theta) + j \cdot Z_L \cdot \sin(\theta)} & \frac{Z_T \cdot Z_L}{Z_T \cdot \cos(\theta) + j \cdot Z_L \cdot \sin(\theta)} \\ \frac{Z_T \cdot Z_L}{Z_T \cdot \cos(\theta) + j \cdot Z_L \cdot \sin(\theta)} & \frac{Z_T \cdot Z_L \cdot \cos(\theta)}{Z_T \cdot \cos(\theta) + j \cdot Z_L \cdot \sin(\theta)} \end{bmatrix}$$

$$V_1 = \begin{cases} V_{ds} \cdot \left( \frac{\xi \cdot \xi_b \cdot \cos(\theta) + j \cdot \xi \cdot \sin(\theta)}{\cos(\theta) + j \cdot \xi_b \cdot \sin(\theta)} \right), & 0 < \xi < \xi_b \\ V_{ds} \cdot \left( \frac{\xi \cdot \xi_b \cdot \cos(\theta) + j \cdot \xi \cdot \sin(\theta)}{\cos(\theta) + j \cdot \xi_b \cdot \sin(\theta)} \right), & \xi_b < \xi < 1 \end{cases}$$

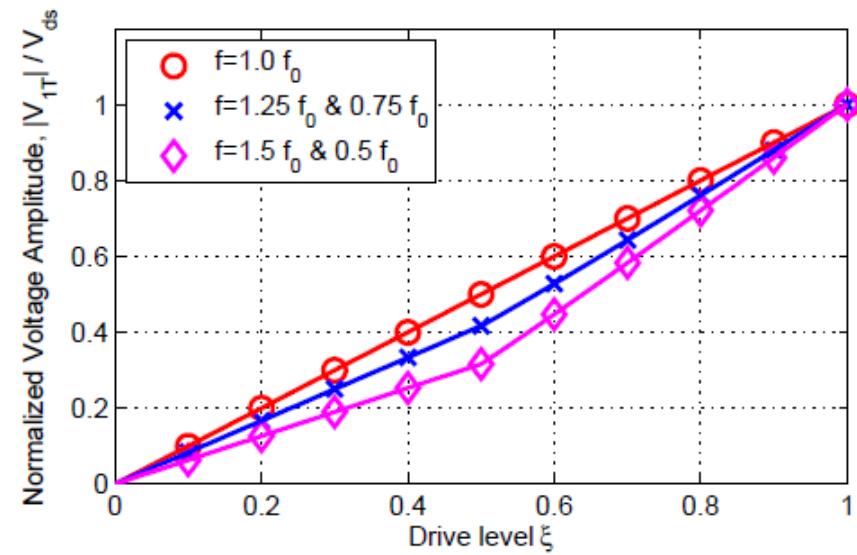
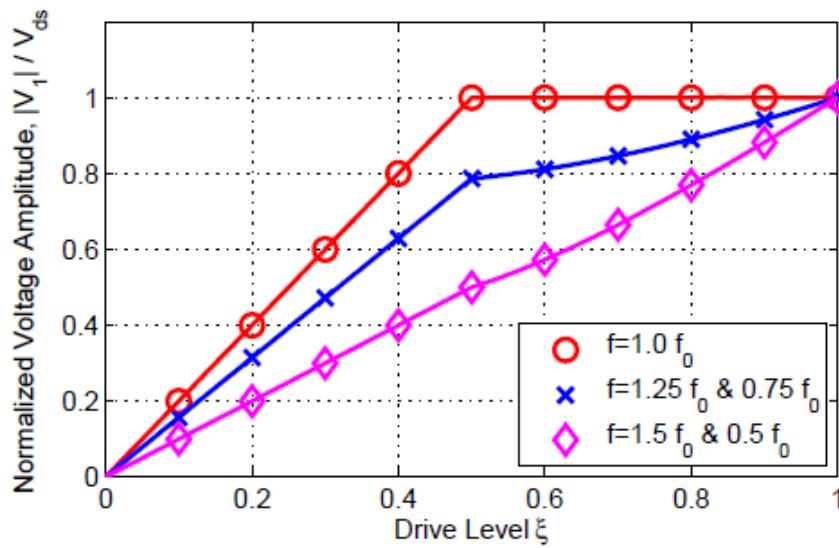
$$V_{1T} = \begin{cases} V_{ds} \cdot \left( \frac{\xi \cdot \xi_b}{\cos(\theta) + j \cdot \xi_b \cdot \sin(\theta)} \right), & 0 < \xi < \xi_b \\ V_{ds} \cdot \left( \frac{\xi \cdot \xi_b + (\xi - \xi_b) \cdot \cos(\theta) \cdot (\cos(\theta) - j \cdot \sin(\theta))}{\cos(\theta) + j \cdot \xi_b \cdot \sin(\theta)} \right), & \xi_b < \xi < 1 \end{cases}$$




# Frequency Response of Ideal Doherty PA(2)

**MACOM**
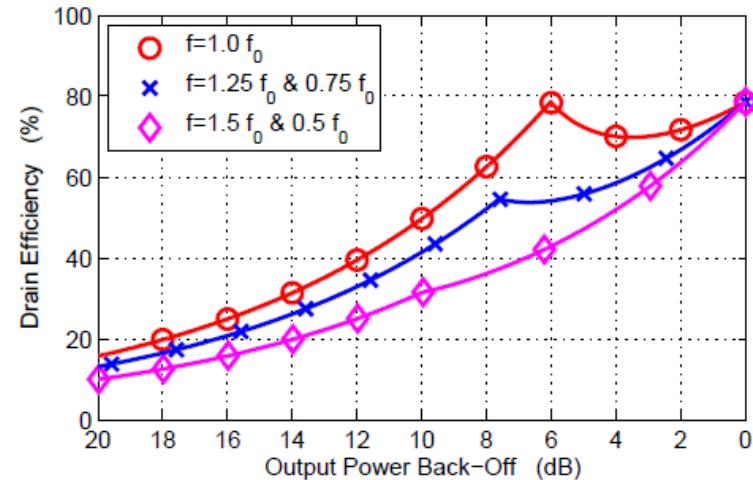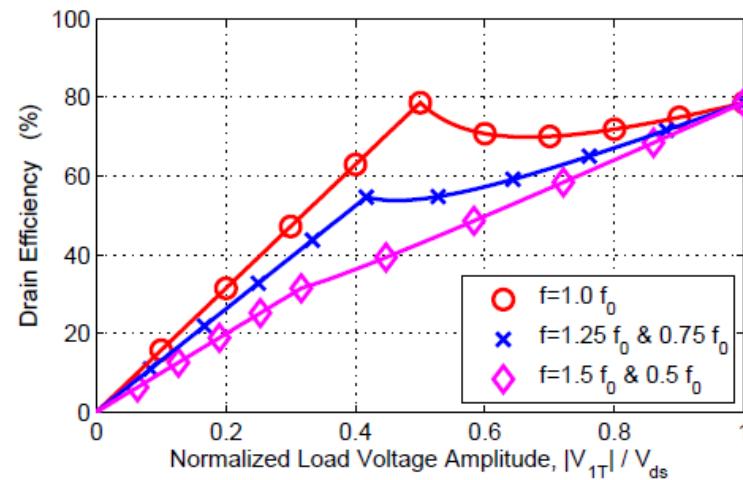
## Frequency Response of Symmetrical Ideal Doherty



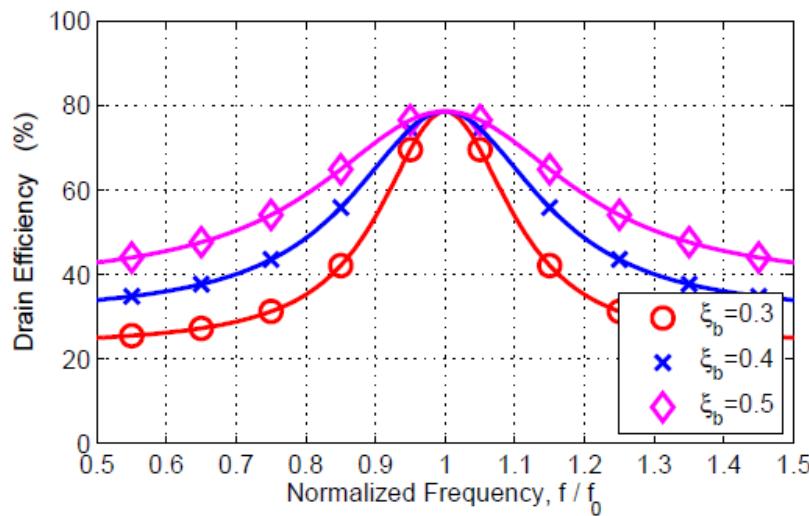The more BO is, the narrower BO efficiency bandwidth is




$\xi_b$	$P_{bo}$	$BW_{\eta-1dB}$
0.30	10.5 dB	14%
0.35	9.1 dB	18%
0.40	8.0 dB	23%
0.45	6.9 dB	28%
0.50	6.0 dB	34%

# A Real Doherty Circuit Diagram

**MACOM**
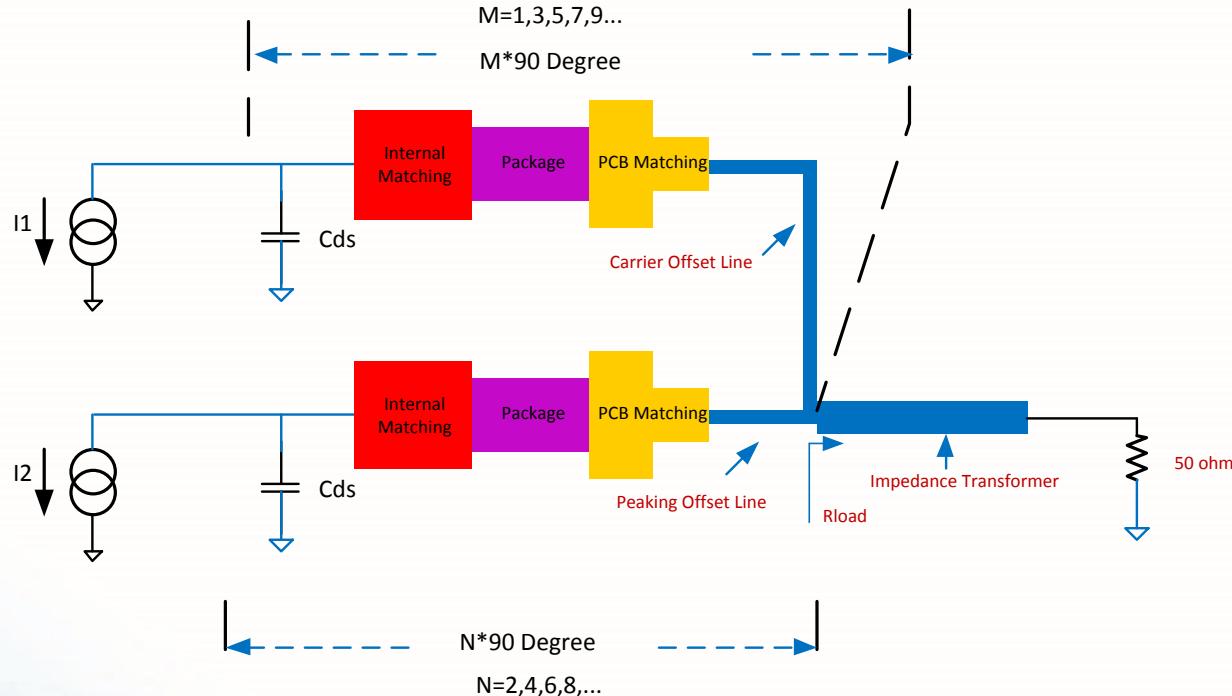
## Low Frequency Doherty Using Discrete Transistor



In MMIC design, Choose  $M=1, N=0$

## High Frequency MMIC Doherty Design




Company Confidential, Internal Use Only


# Topologies Of Impedance Inverting Network (1)

**MACOM**

## Impedance Inverting Network

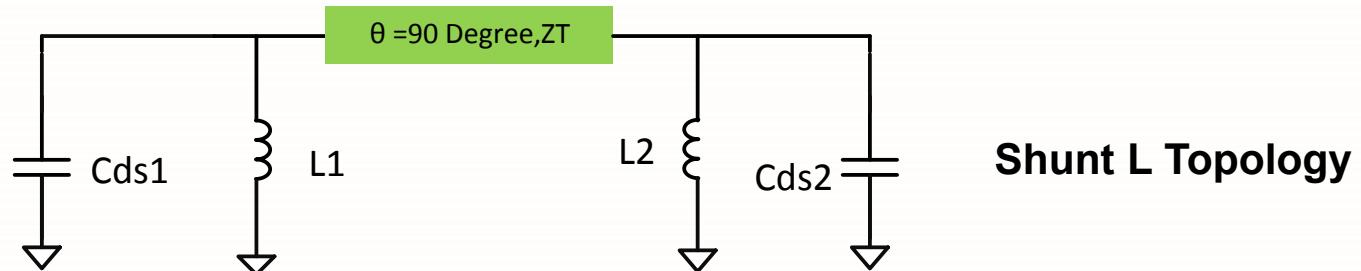

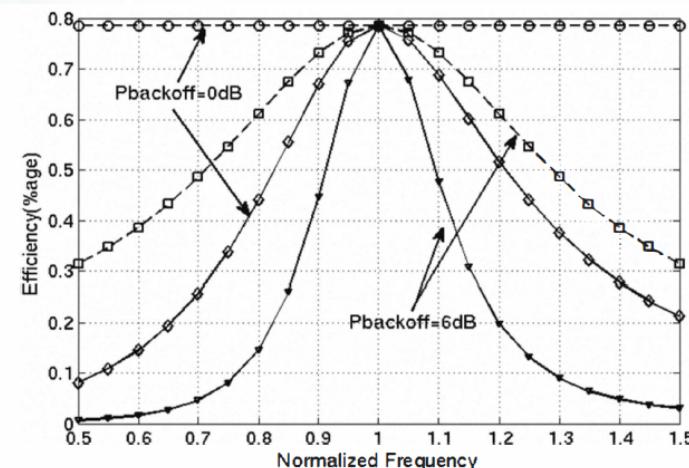1. For MMIC Design, For low or medium power, ZT will larger than 100 ohm, The strip line on die is difficult to be realized
2. L1 and L2 are very difficult to be realized because of DC current handling;
3. Reduce the bandwidth;



Dash Line: DPA without Cds;  
Solid Line: DPA with Cds and using Shunt L

# Topologies Of Impedance Inverting Network (2)

**MACOM**

## Impedance Inverting Network




$$\theta_n = \arccos(\omega_0 \cdot C_{out} \cdot Z_T)$$

$$Z_n = \frac{Z_T}{\sin(\theta_n)}$$

## Quasi-lumped network


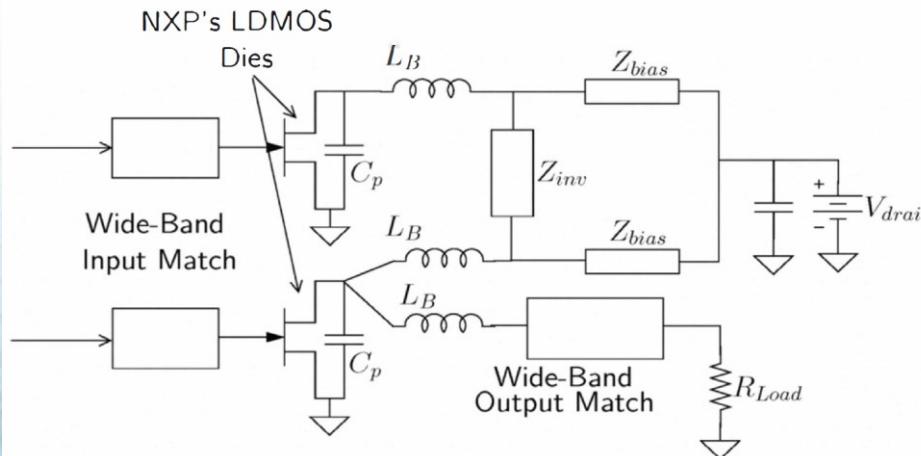
1. The topology can absorb the  $C_{ds}$  and bond wires into the impedance inverter;
2. When  $Z_T$  is high,  $Z_n$  is very small, maybe difficult to realize
3. Additional Bias network is needed



Reference: J. Qureshi, N. Li, W. Neo, F. van Rijs, I. Blednov, and L.de Vreede, "A Wide-Band 20W LMOS Doherty Power Amplifier," in 2010 IEEE MTT-S Int. Microwave Symp. Dig., may 2010, pp. 1504-1507.

# Topologies Of Impedance Inverting Network (3)

MACOM

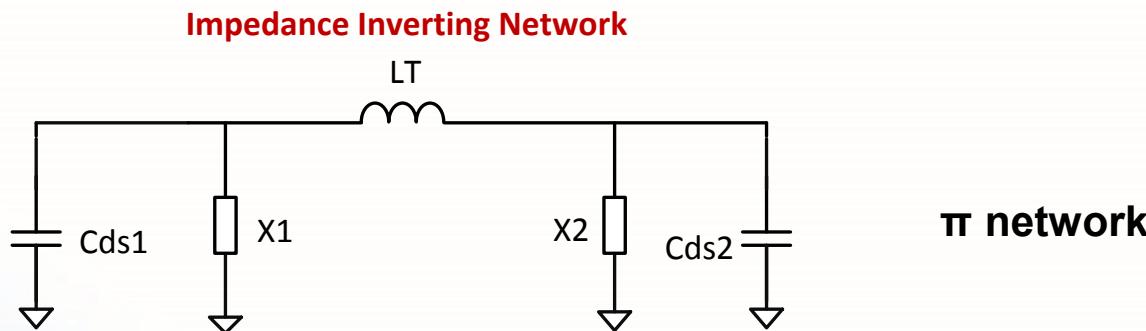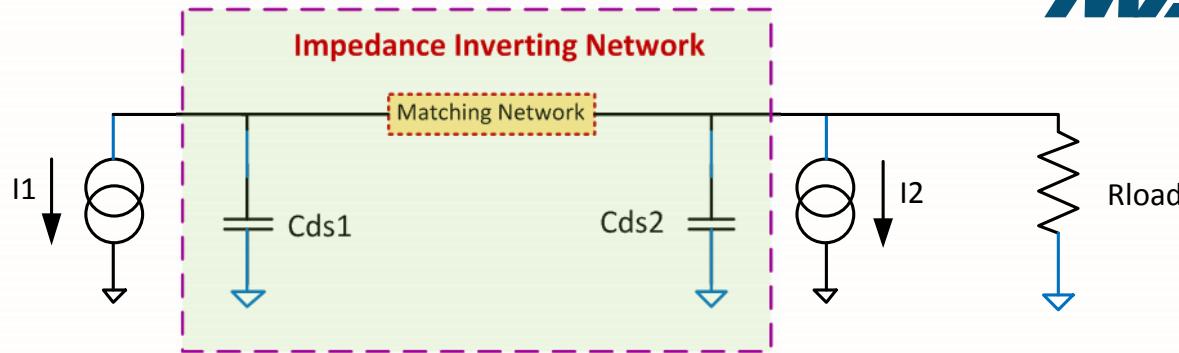

$$X_i = \frac{1}{\omega_0 \cdot (C_{out,i} - C_T)}$$







$$C_T = \frac{1}{\omega_0 \cdot Z_T} \quad L_T = \frac{Z_T}{\omega_0}$$

1.  $L_T$  maybe too large to be realized in MMIC process

# Topologies Of Impedance Inverting Network (4)

**MACOM**


Impedance Inverting Network

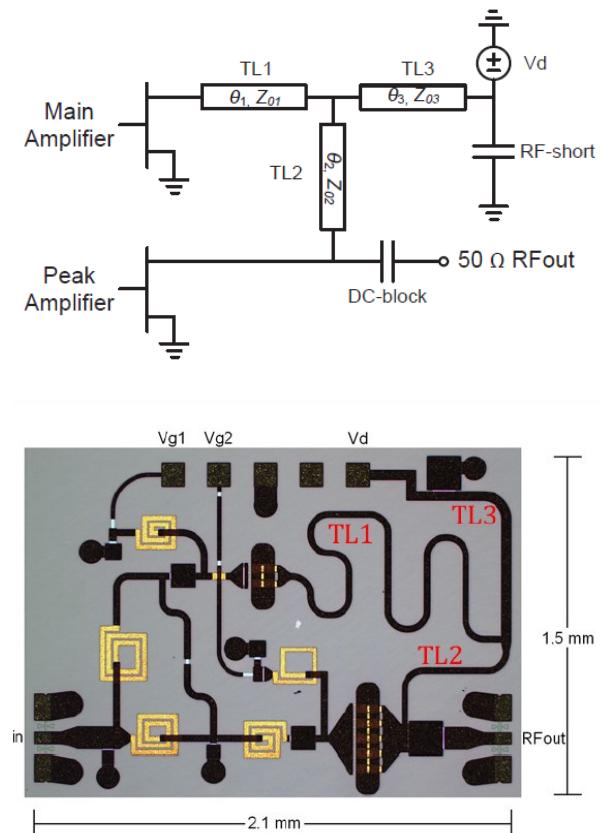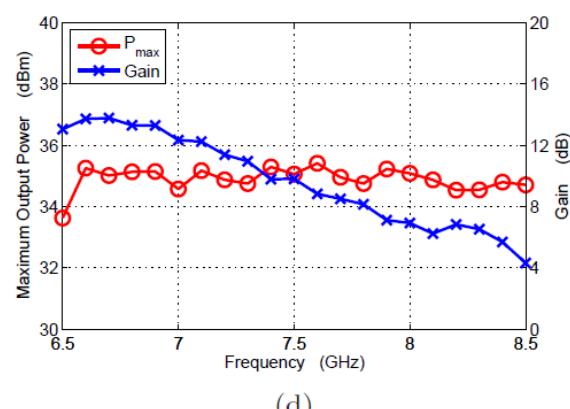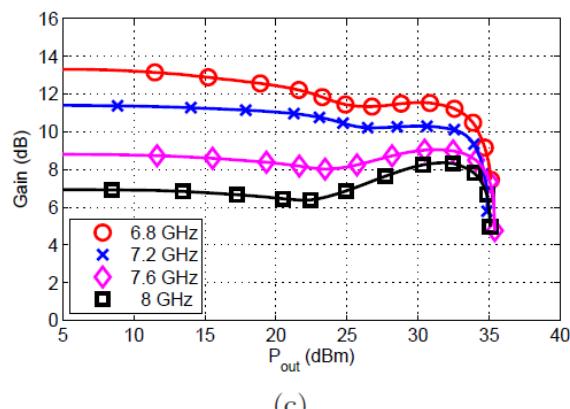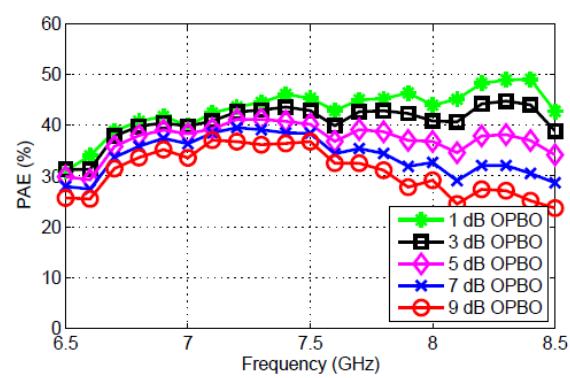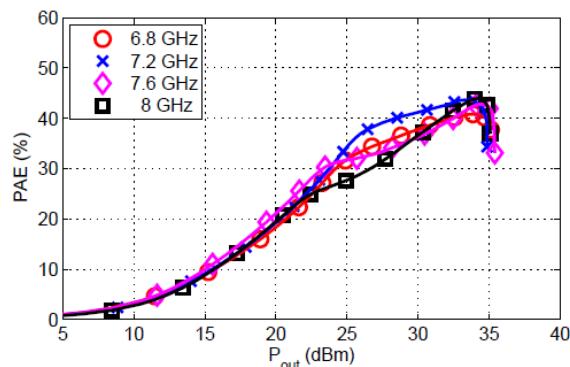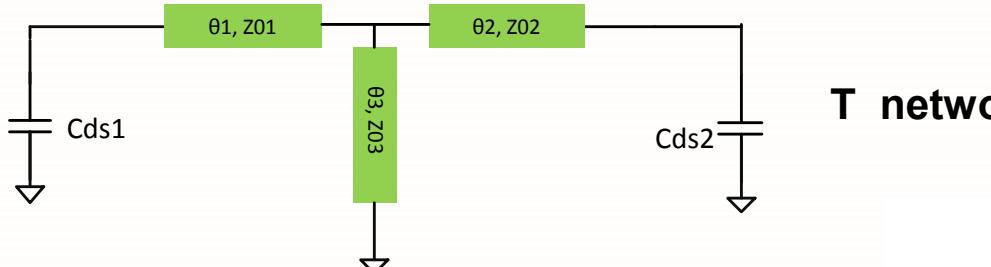


# Off State performance of Peaking Amplifier (1)

**MACOM**
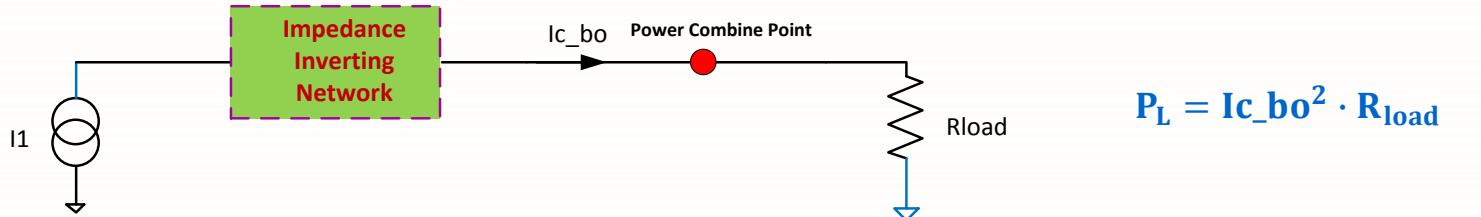
## 1. When No Off State Peaking Amplifier Connected To The High Load Carrier Amplifier


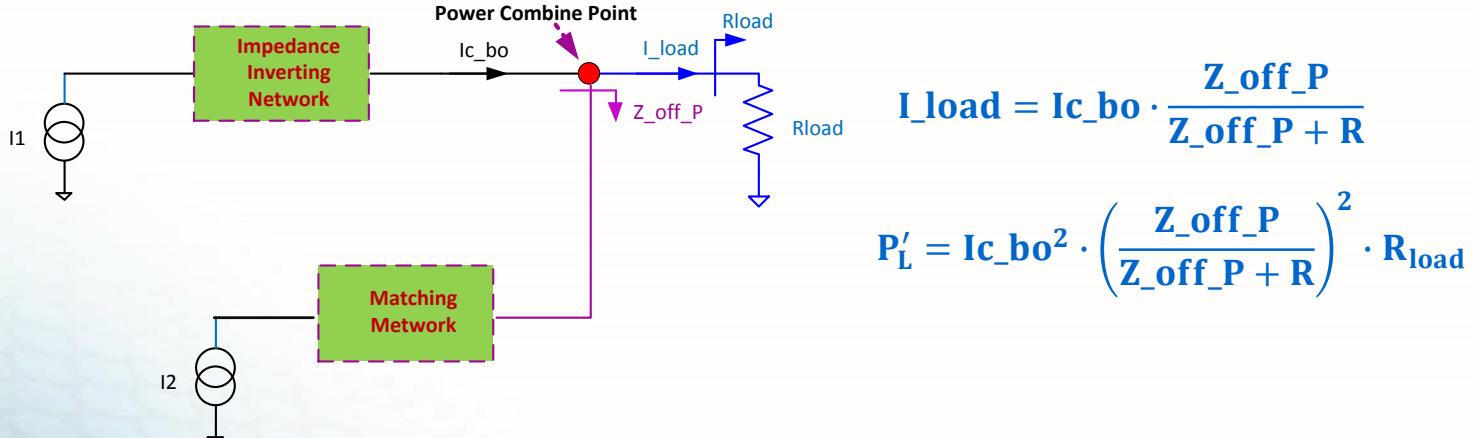
## 2. Then Adding The Off State Peaking Amplifier To The High Load Carrier Amplifier (Assuming Adding Off State Peaking Do Not Affect The Impedance Too Much)




## 3. Then the Transducer Loss can be calculated:

$$TL = 10 \cdot \log \left( \frac{P'_L}{P_L} \right) = 10 \cdot \log \left( \frac{P'_L}{P_L} \right) = 10 \cdot \log \left( \frac{Z_{off\_P}}{Z_{off\_P} + R} \right)^2 = -20 \cdot \log \left( \frac{Z_{off\_P} + R}{Z_{off\_P}} \right) = -20 \cdot \log \left( 1 + \frac{R}{Z_{off\_P}} \right)$$

# Off State performance of Peaking Amplifier (2)

**MACOM**
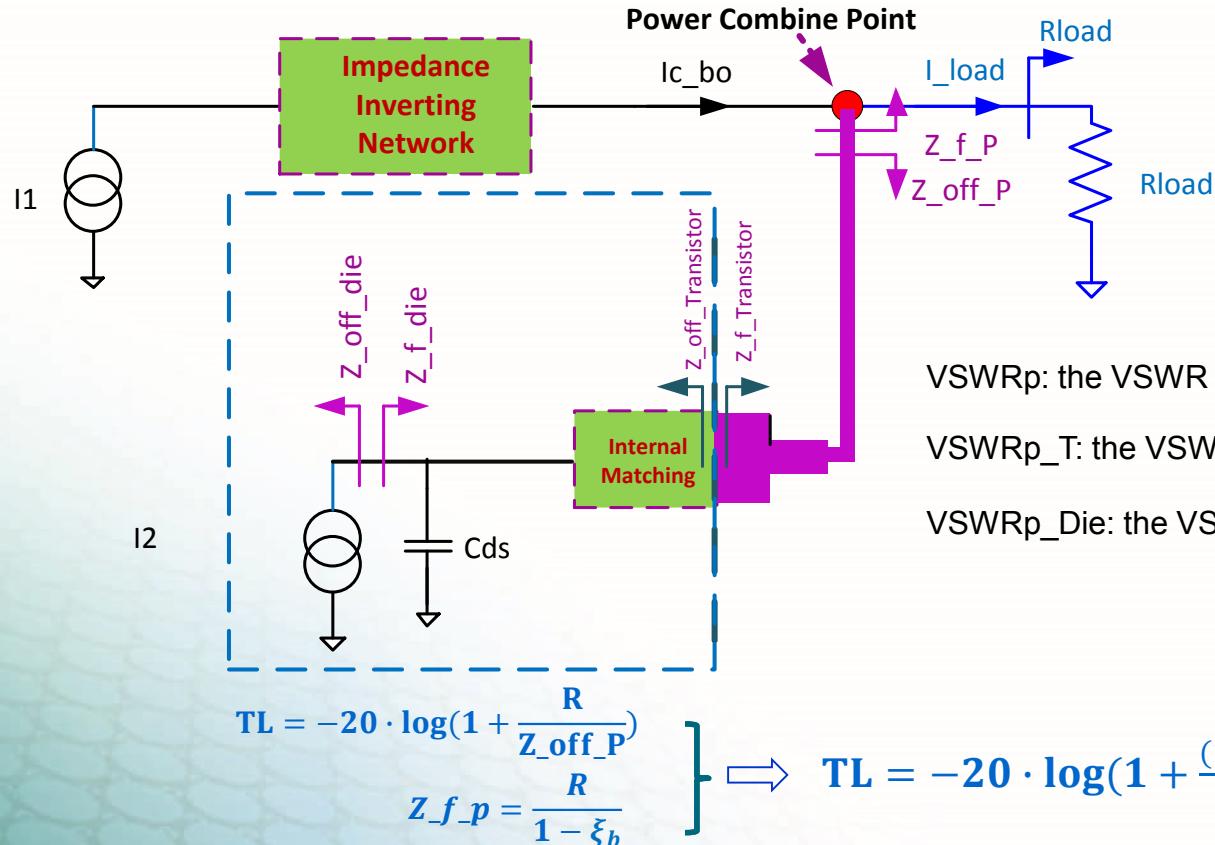
## 4. The Relationship Between TL, VSWRp and VSWRp\_T



VSWRp: the VSWR between  $Z_{f\_p}$  and  $Z_{off\_P}$

VSWRp\_T: the VSWR between  $Z_{f\_Transistor}$  and  $Z_{off\_Transistor}$

VSWRp\_Die: the VSWR between  $Z_{f\_Die}$  and  $Z_{off\_Die}$


If assuming PCB matching is lossless, then

$$TL = -20 \cdot \log\left(1 + \frac{1 - \xi_b}{VSWRp_T}\right)$$


The VSWRp\_T can be called ***the figure of merit*** for off state peak performance

# Off State performance of Peaking Amplifier (3)

**MACOM**

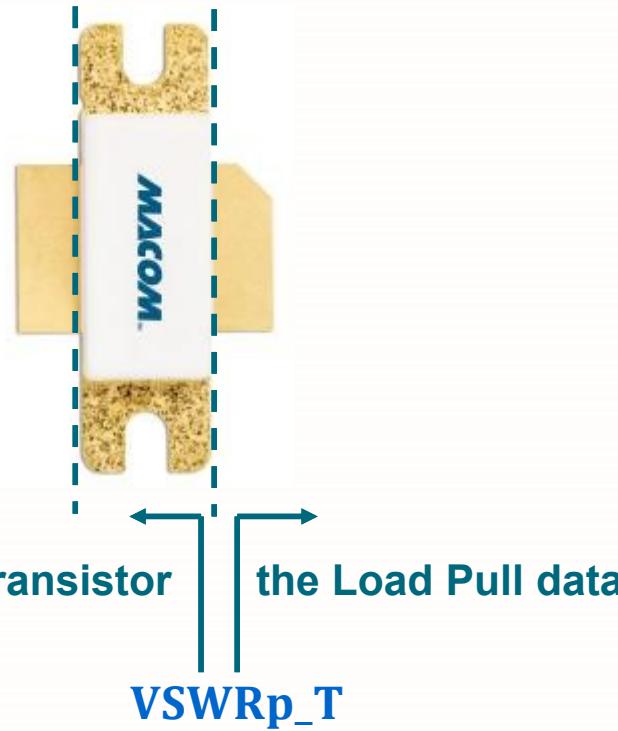


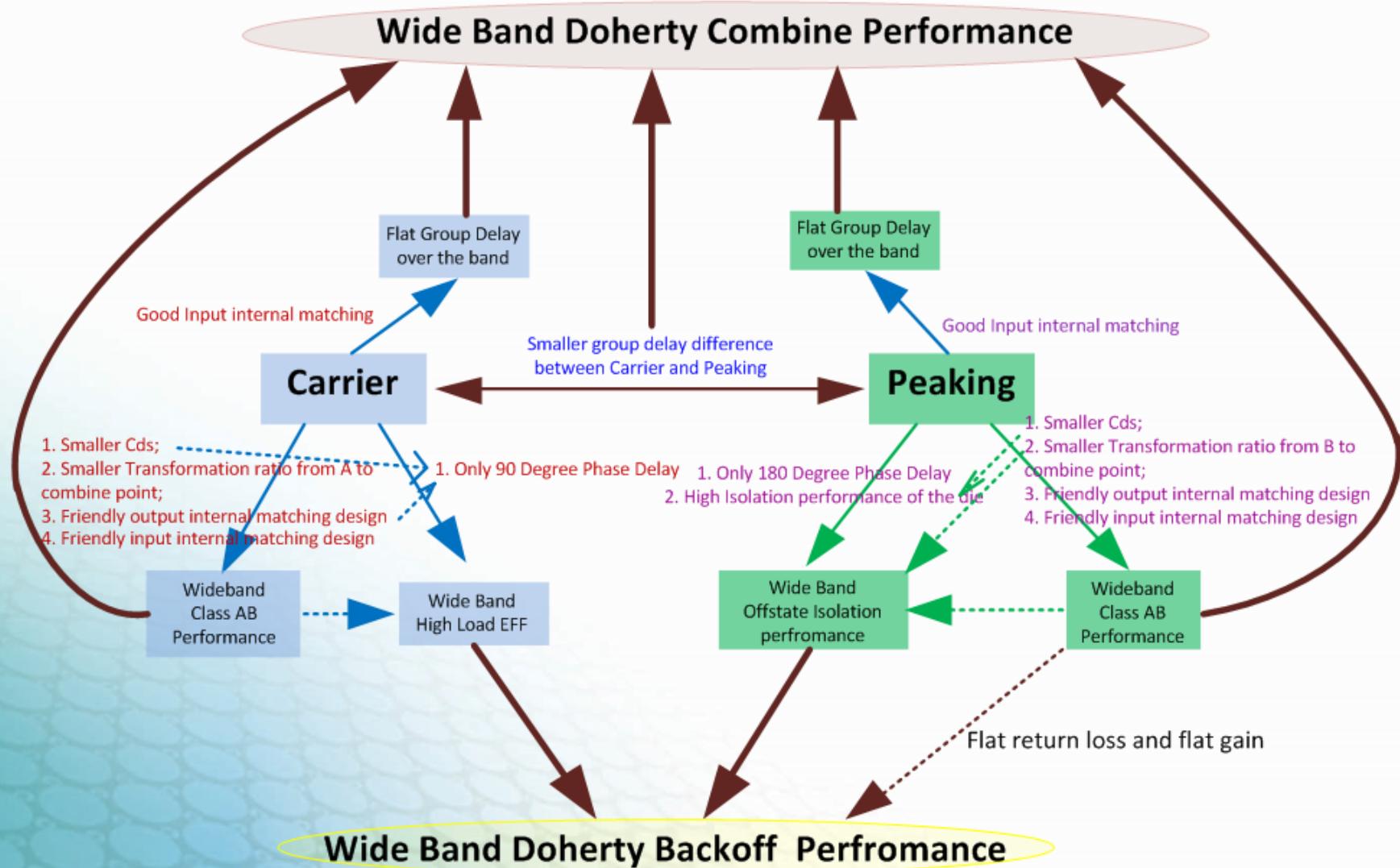1. Choosing PCB matching impedance close to the MXP point will get better off state performance
2. Loss between the Die and Power combine point will degrade the off state performance,  
So zero phase delay is highly recommended rather than 180 degree phase delay in peaking amplifier design




# 'N Way' Doherty

**MACOM**

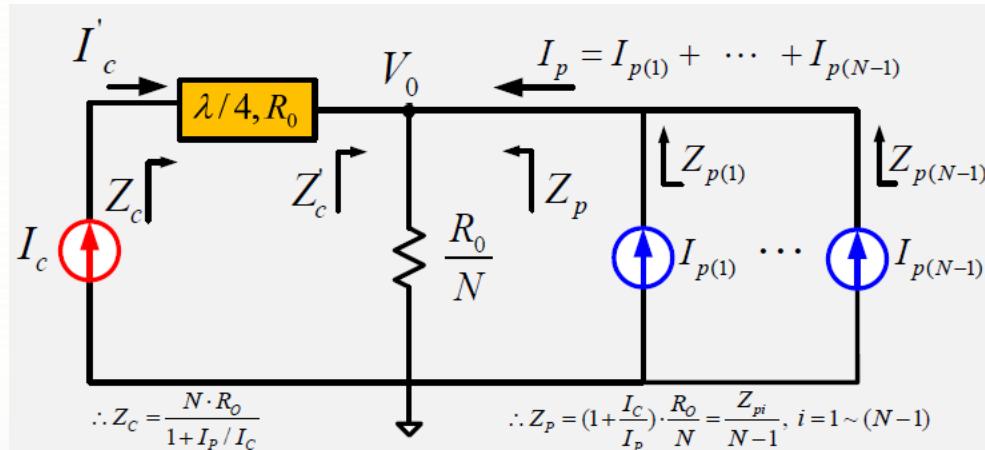

Be called 'N way' Doherty



Also be called Asymmetrical Doherty

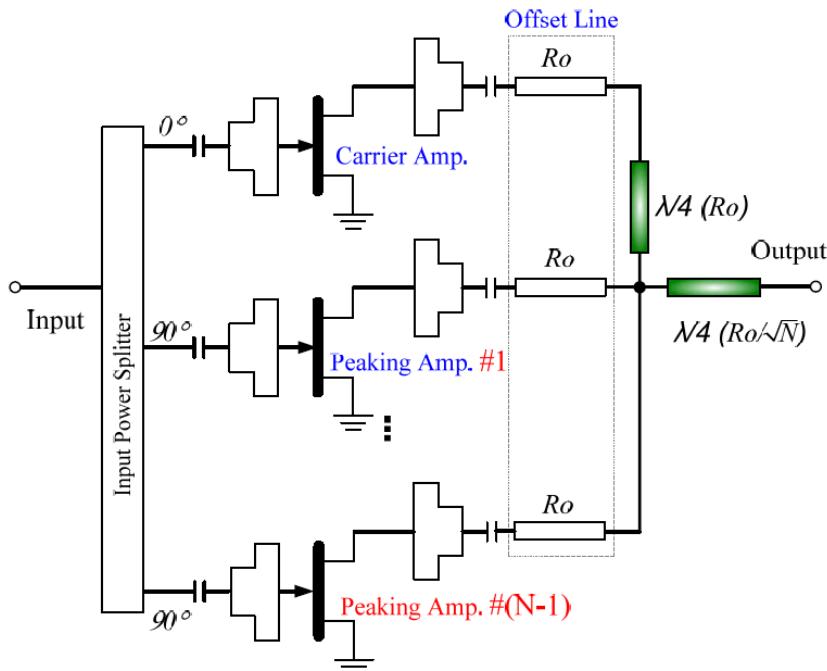

1. N+1:1 load modulation for Carrier Amplifier
2. All N peaking amplifier be turned on at the same time
3. Bandwidth is limited by the high load modulation
4. EFF will drop a lot between the two MAX EFF points

# Conventional 3-stage Doherty Amplifier

MACOM

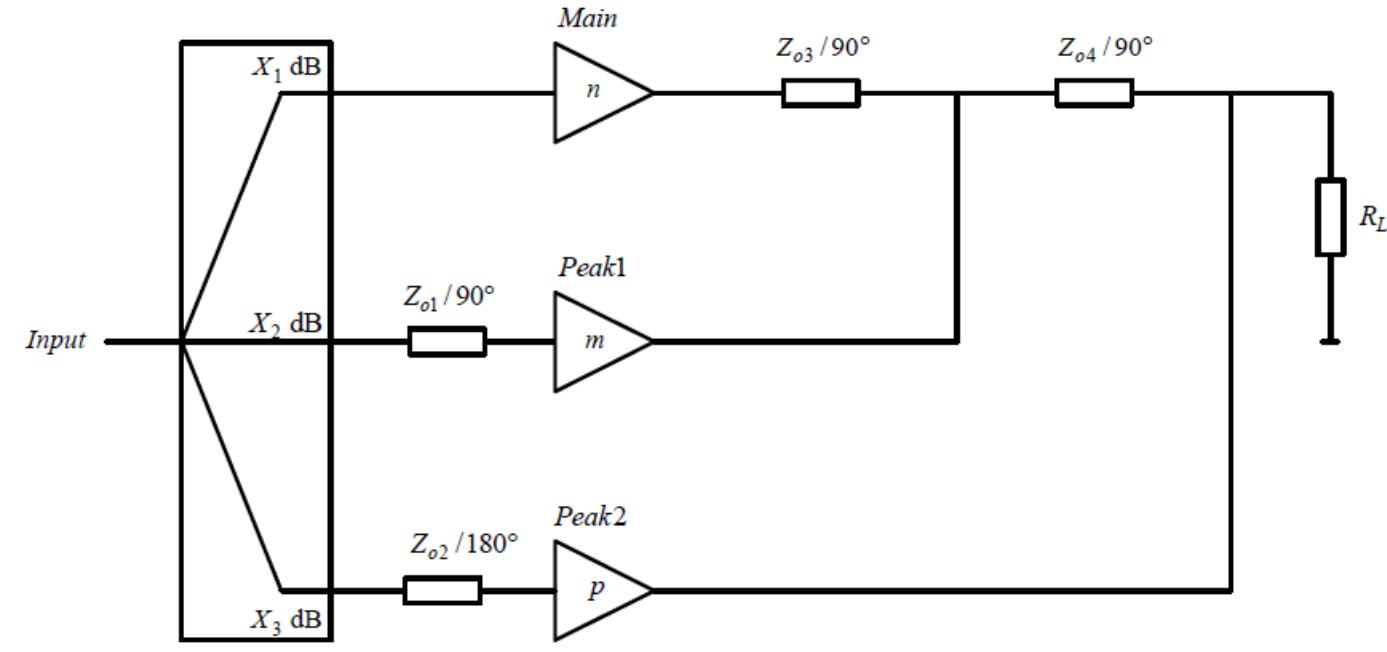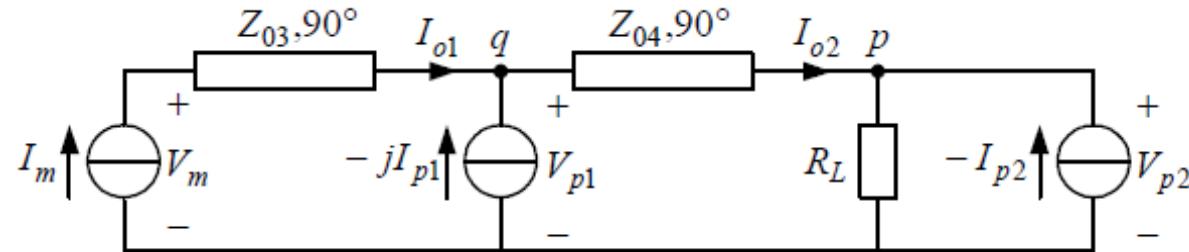

Can be seen as One Doherty Amplifier + an additional peaking amplifier


# Conventional 3-stage Doherty Amplifier

**MACOM**

If the MAX power of the carrier, 1<sup>ST</sup> peaking and 2<sup>ND</sup> peaking amplifier are given,  
The BO point (k1, k2 ) can be determined by the following equation:

$$k_2 = \frac{P_{\max\_c}}{P_{\max\_c} + P_{\max\_P1}} \quad k_1 = \frac{P_{\max\_c} + P_{\max\_P1}}{P_{\max\_c} + P_{\max\_P1} + P_{\max\_P2}} \quad P_{\max\_c}:P_{\max\_c}:P_{\max\_c}=k_1k_2:k_1(1-k_2):(1-k_1)$$


---

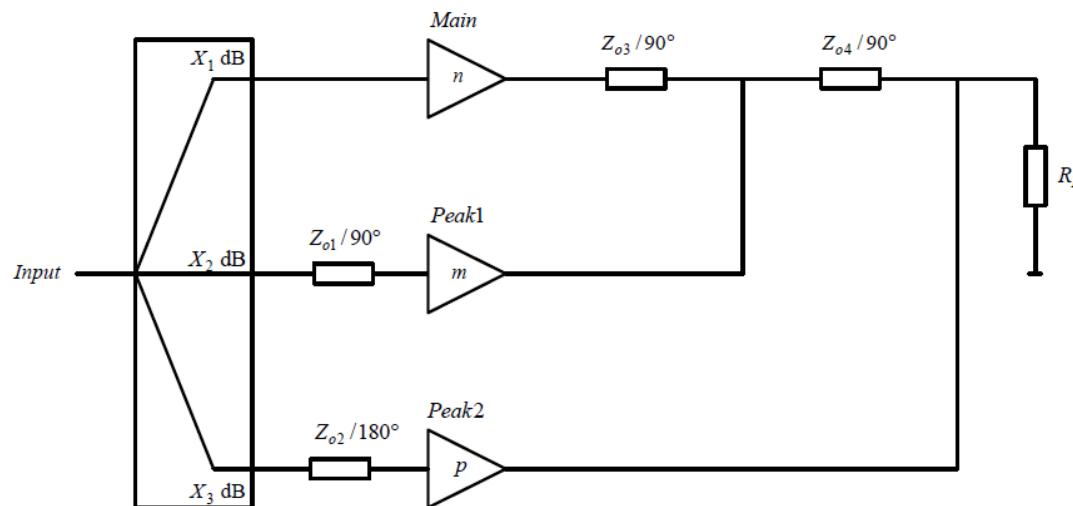

$$Z_{o3} = \sqrt{\frac{Z_{mF} \cdot Z_{p1F} \cdot (1 - k_2)}{k_2}}$$

$$Z_{o4} = \sqrt{\frac{Z_{p1F} \cdot Z_{p2F} \cdot (1 - k_1) \cdot (1 - k_2)}{k_2}}$$

$$R_L = Z_{p2F} \cdot (1 - k_1)$$

Load line modulation factor of carrier PA is:

$$VSWR = \frac{k_1}{k_2}$$


# Conventional 3-stage Doherty Amplifier

**MACOM**

$$R_{mL} = R_{p1L} = R_{p2L} = 50\Omega$$

	P <sub>main</sub>	P <sub>peak1</sub>	P <sub>peak2</sub>	10log(k <sub>2</sub> <sup>2</sup> )	10log(k <sub>1</sub> <sup>2</sup> )	Z <sub>03</sub> Ohm	Z <sub>04</sub> Ohm	R <sub>L</sub> Note 1	VSWR_main
k <sub>1</sub> =1/2,k <sub>2</sub> =1/4	1	3	4	-12dB	-6dB	86.6	43.3	25	2
k <sub>1</sub> =4/7,k <sub>2</sub> =1/4	1	3	3	-12dB	-4.9dB	86.6	37.5	21.4	2.3
k <sub>1</sub> =3/5,k <sub>2</sub> =1/3	1	2	2	-9.5dB	-4.4dB	70.7	33.3	20	1.8
k <sub>1</sub> =2/3,k <sub>2</sub> =1/2	1	1	1	-6dB	-3.5dB	50	25	16.7	1.33

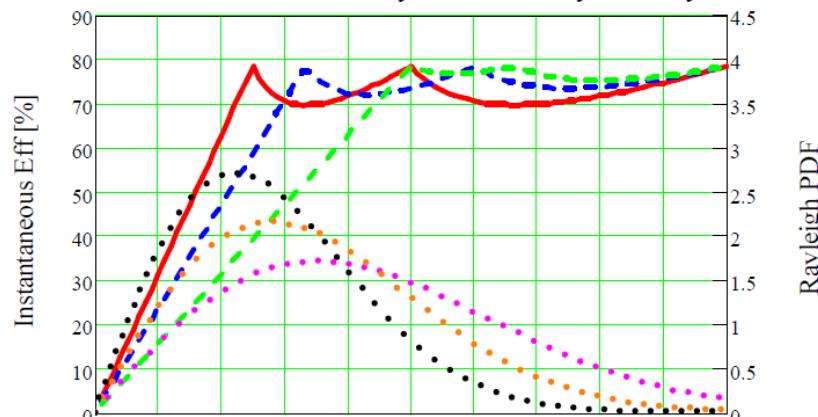
Instantaneous Efficiency of Three-way Doherty



Normalized Output Voltage

- 3-Way Doherty (1:3:4)
- 3-Way Doherty (1:2:2)
- 3-Way Doherty (1:1:1)
- PAR = 6dB
- PAR = 8dB
- PAR = 10dB

Average Efficiency of Three-way Doherty

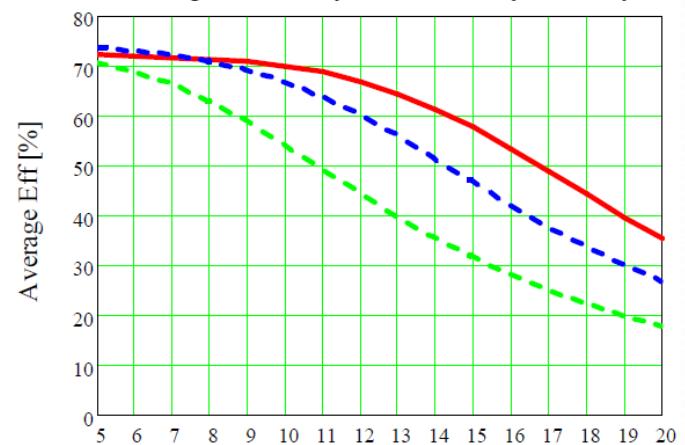


Peak-to-Average\_Ratio [dB]

- 3-Way Doherty (1:3:4)
- 3-Way Doherty (1:2:2)
- 3-Way Doherty (1:1:1)

# Issues of Conventional 3-stage Doherty Amplifier


**MACOM**

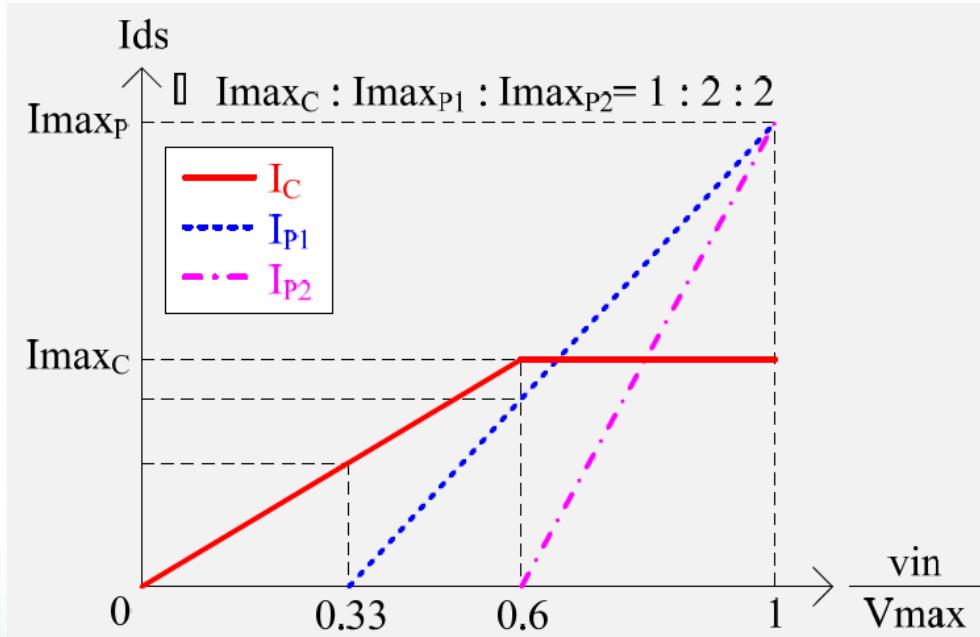

1. The load line of Carrier amplifier stops at a certain power level causing heavy saturation of the carrier device, And will also cause gate current flow for GaN HEMT;
2. If better modulated signal back off efficiency achieved than using 2 way Doherty, different size of transistor will Be used in carrier, peaking1 and peaking2 amplifier

# Novel 3-stage Doherty Amplifier

**MACOM**

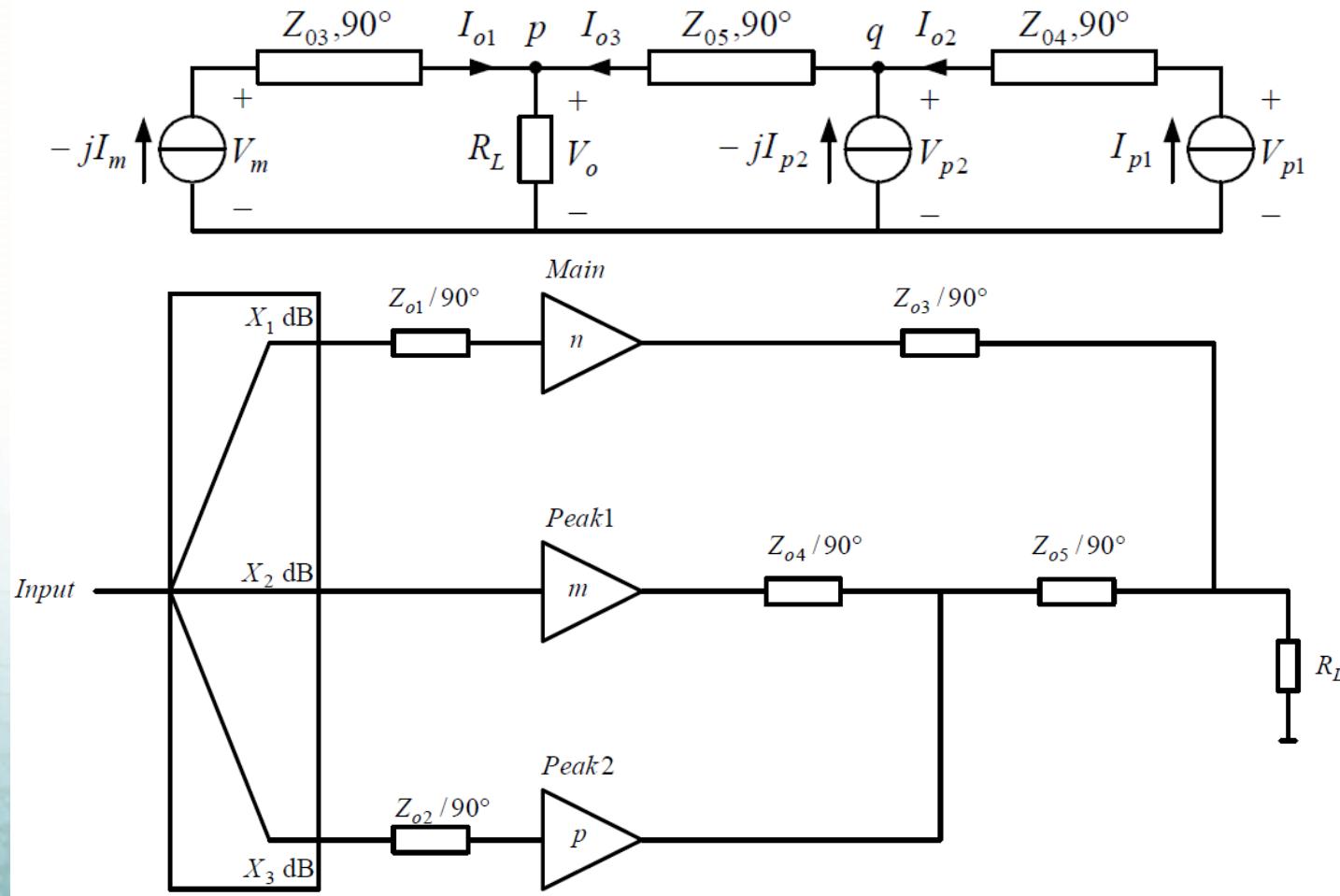

Can be seen as One Carrier Amplifier + an additional Doherty Amplifier working as a peaking amplifier


# Novel 3-stage Doherty Amplifier

**MACOM**

If the MAX power of the carrier, 1<sup>ST</sup> peaking and 2<sup>ND</sup> peaking amplifier are given,  
The BO point (k<sub>1</sub>, k<sub>2</sub>) can be determined by the following equation:

$$k_1 = \frac{P_{\max\_p1}}{P_{\max\_p1} + P_{\max\_p2}} \quad k_2 = \frac{P_{\max\_c}}{P_{\max\_c} + P_{\max\_p1} + P_{\max\_p2}}$$
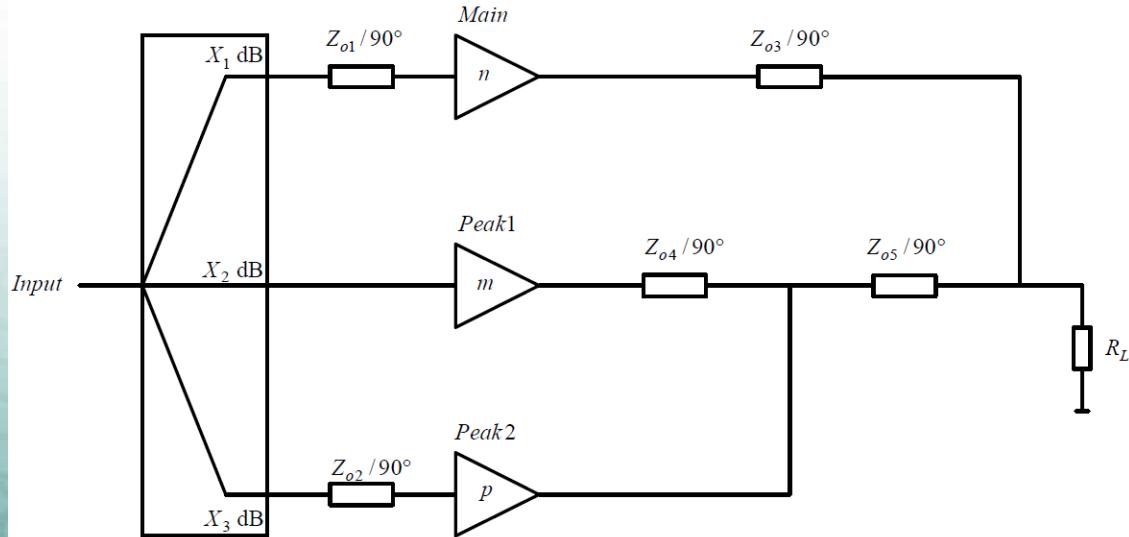
$$P_{\max\_c}:P_{\max\_p1}:P_{\max\_p2} = k_2:k_1(1-k_2):(1-k_1)(1-k_2)$$



$$Z_{03} = \sqrt{\frac{R_{L-f}R_L}{k_2}}$$

$$Z_{05} = Z_{03} \cdot \left( \frac{k_2}{1 - k_2} \right)$$

$$Z_{04} = \frac{R_{L-f}}{k_1} \left( \frac{k_2}{1 - k_2} \right)$$

Load line modulation factor of carrier PA is:



$$VSWR = \frac{1}{k_2}$$

# Novel 3-stage Doherty Amplifier

**MACOM**

$$R_{m\_L} = R_L = 50\Omega$$

	P <sub>M_1dB</sub> (W)	P <sub>P1_1dB</sub> (W)	P <sub>P2_1dB</sub> (W)	10log(k <sub>2</sub> <sup>2</sup> )	10log(k <sub>1</sub> <sup>2</sup> )	Z <sub>03</sub> Ohm	Z <sub>04</sub> Ohm	Z <sub>05</sub> Ohm	VSWR_main
k <sub>1</sub> =1/2,k <sub>2</sub> =1/5	(1)	(2)	(2)	-14dB	-6dB	111.8	28	25	5
k <sub>1</sub> =1/2,k <sub>2</sub> =1/4	(2)	(3)	(3)	-12dB	-6dB	100	33.3	33.3	4
k <sub>1</sub> =1/2,k <sub>2</sub> =1/3	(1)	(1)	(1)	-9.5B	-6dB	86.6	50.0	43.3	3

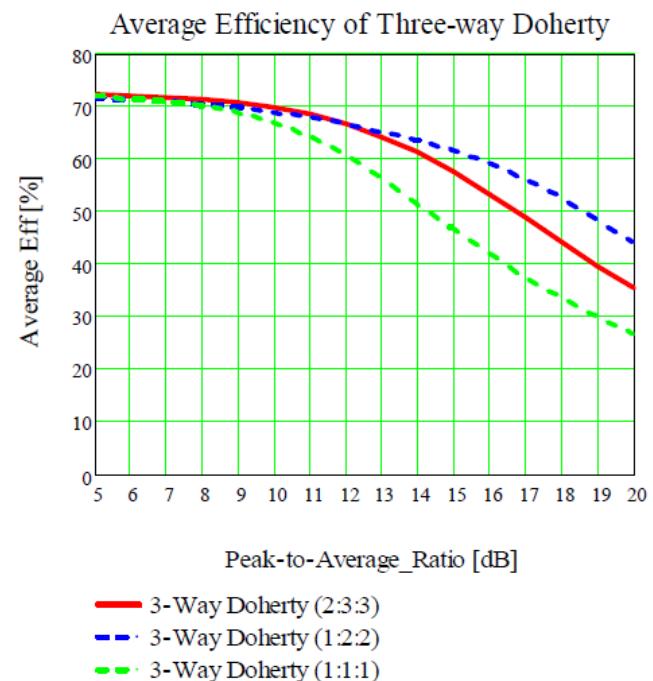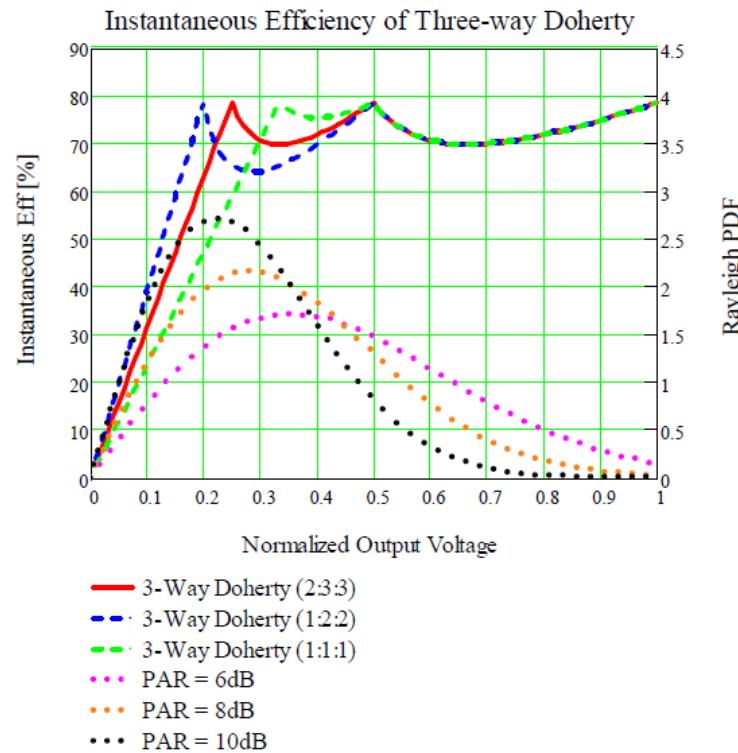

# Comparison Between Conventional and Novel 3-stage Doherty Amplifier


**MACOM**

## 1. Principle of working:

**Conventional :** Can be seen as One Doherty Amplifier + an additional peaking amplifier


**Novel:** Can be seen as One Carrier Amplifier + an additional Doherty Amplifier working as a peaking amplifier
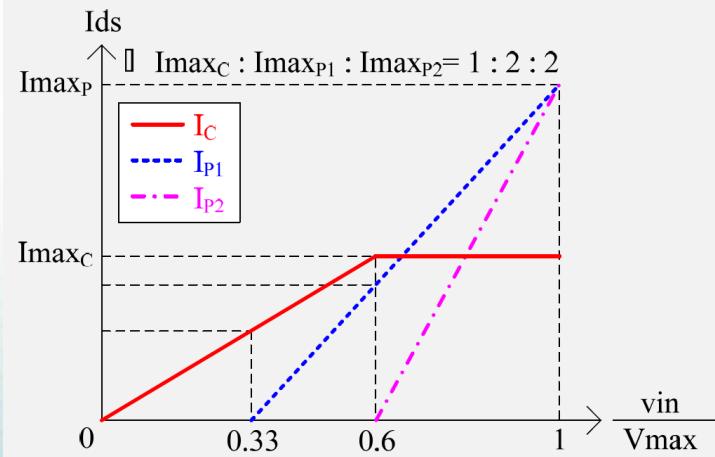
## 2. Current Variation when input power increase:



Load line modulation factor of carrier PA is:

$$VSWR = \frac{k_1}{k_2}$$

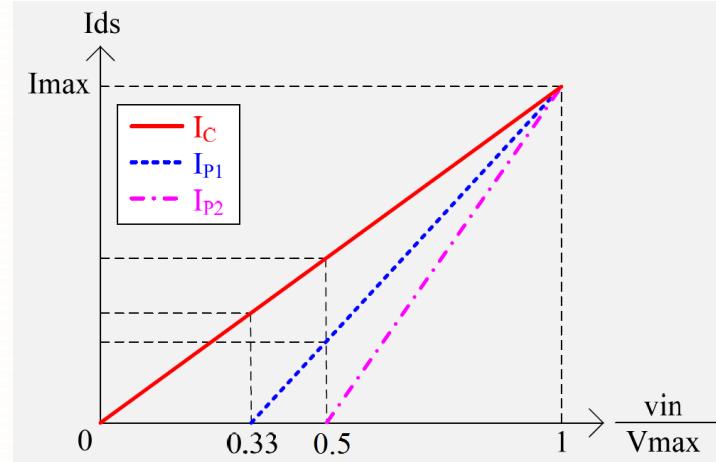

Load line modulation factor of carrier PA is:

$$VSWR = \frac{1}{k_2}$$

# Overview of Doherty Design Template

**MACOM**

Very useful tool for designers who design package asymmetrical Doherty transistors

## Sub Modules in the Template



**Doherty Structure**

- 1. Die Selection Tool;
- 2. Doherty Design Tool;
- 3. Doherty HB Simulation module



**Transistor Design**

- 1. Internal input and output matching design
- 2. Active transistor model build
- 3. Simulated and tested Load pull data analysis




**PCB Matching Design**

- 1. Input and output PCB matching design;

### 3. Introduction of Analysis Tools

**MACOM**





#### 1) Bandwidth Analysis Tool(a)

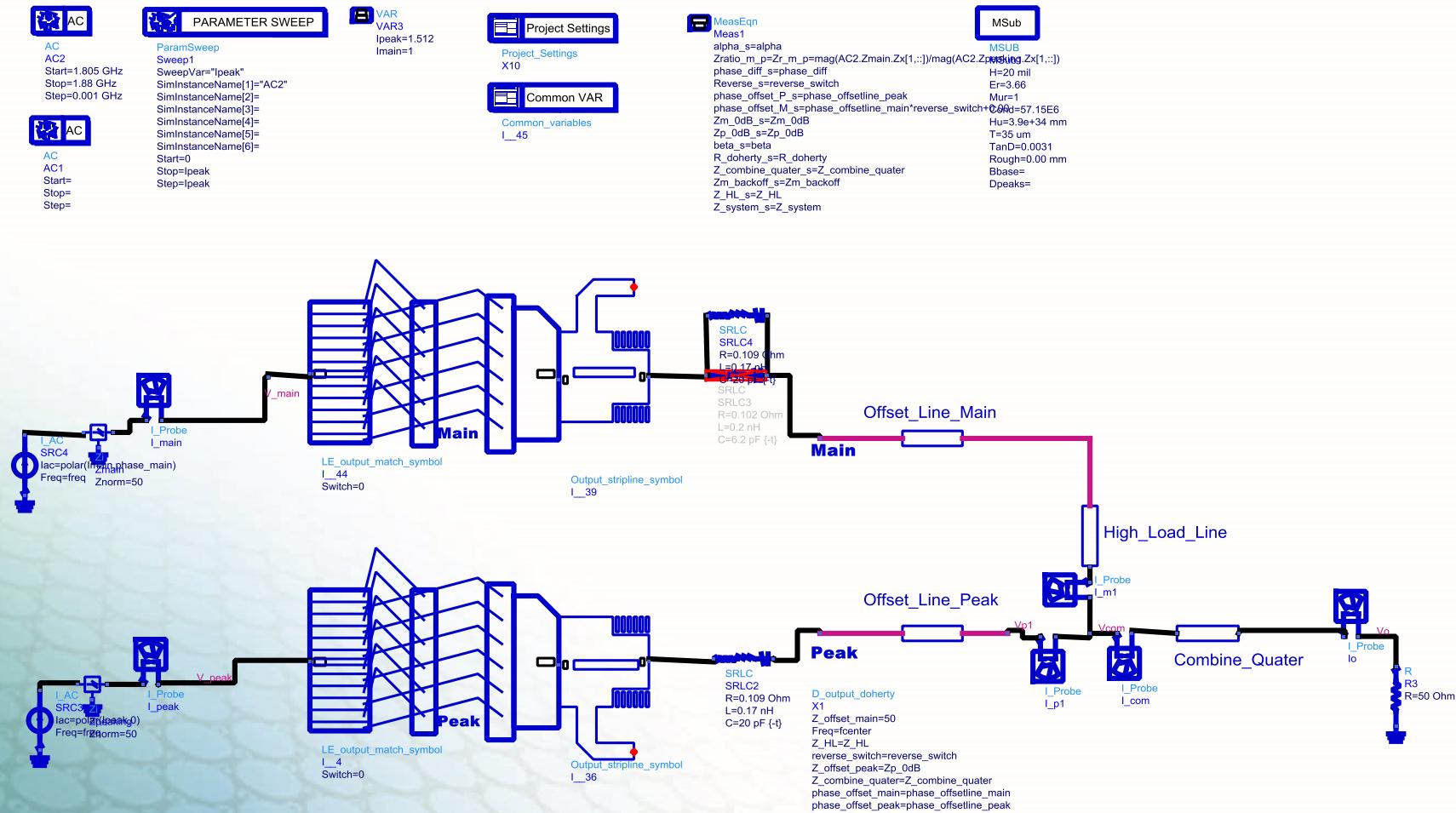

### 3. Introduction of Analysis Tools

**MACOM**

#### 1) Bandwidth Analysis Tool(b)

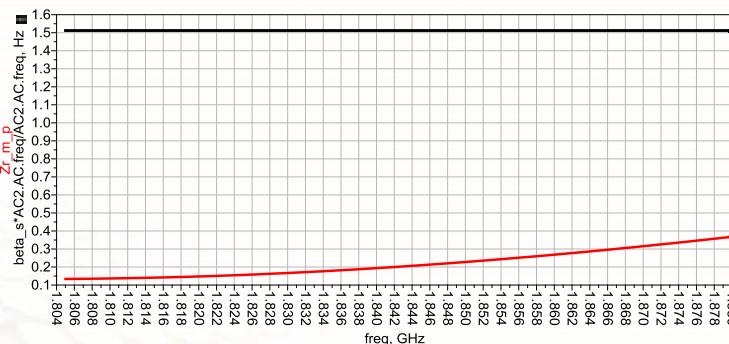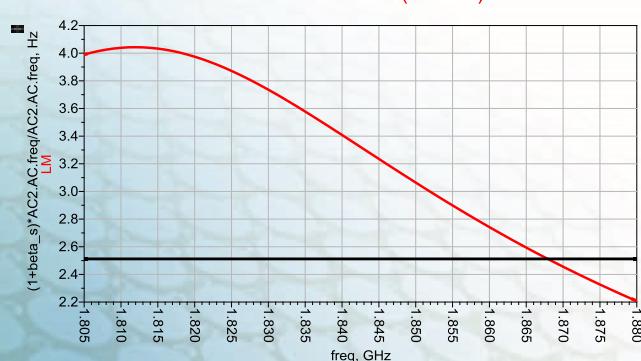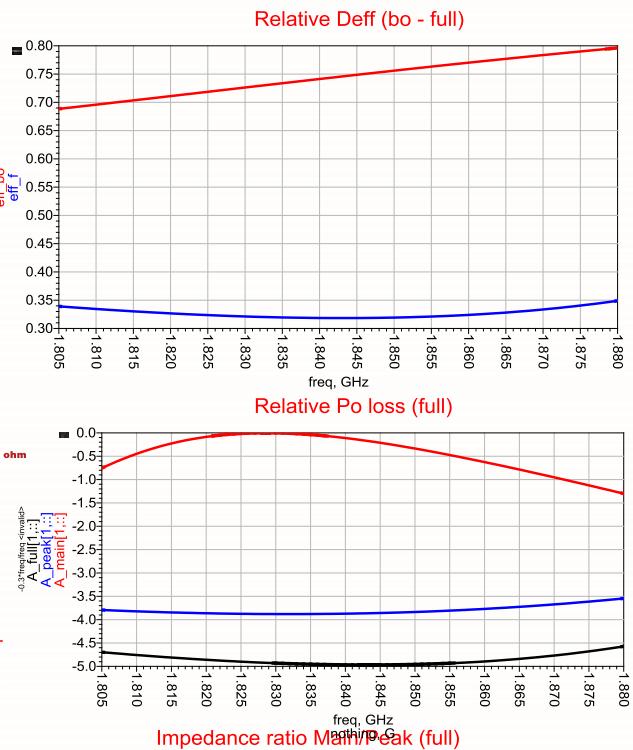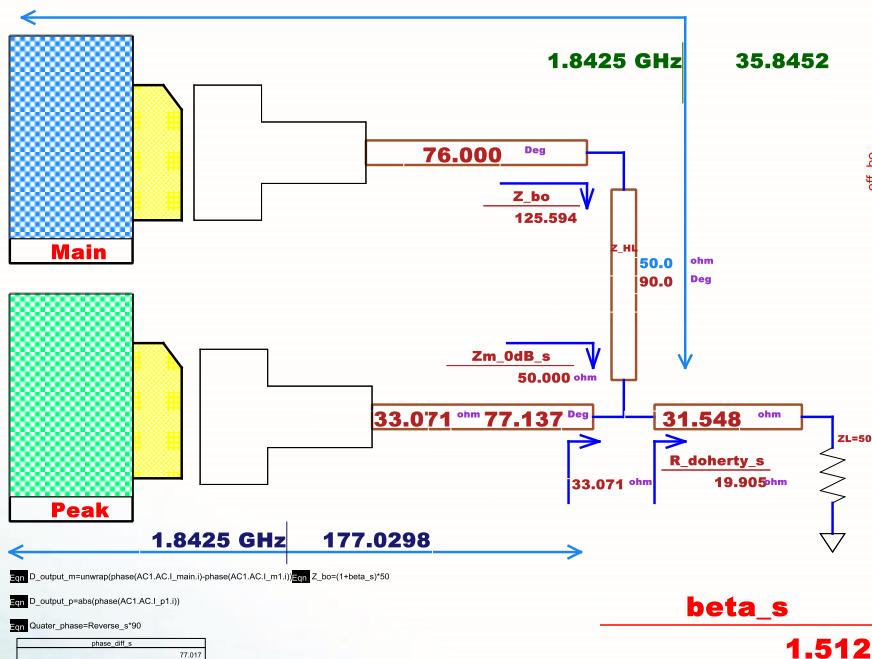




Can calculate the relative bandwidth , the load modulation behavior over the band

### 3. Introduction of Analysis Tools

**MACOM**

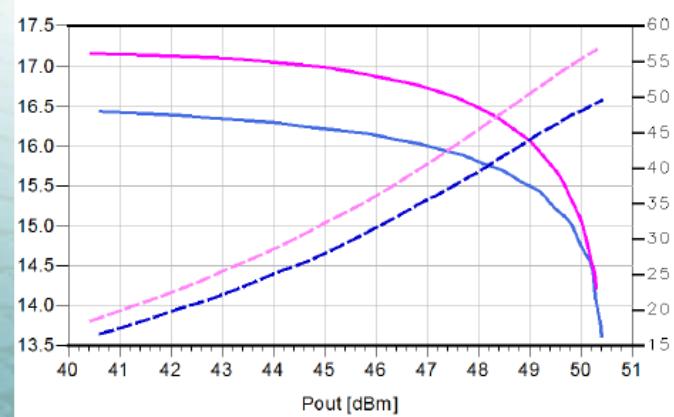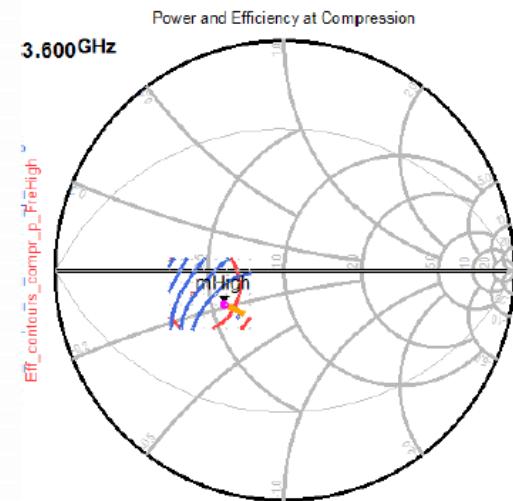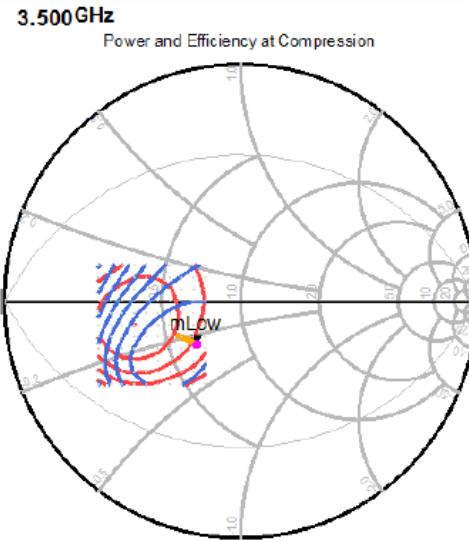2) LP data analysis tool(a),

Can map impedance matching results onto the LP data



	3.500GHz	3.600GHz
Pout	50.40dBm	50.30dBm
Pout	109.56W	107.04W
Eff	49.58%	56.75%





### 3. Introduction of Analysis Tools

**MACOM**

2) LP data analysis tool(b),

Can analysis the high load performance over the band

2:1 High Load

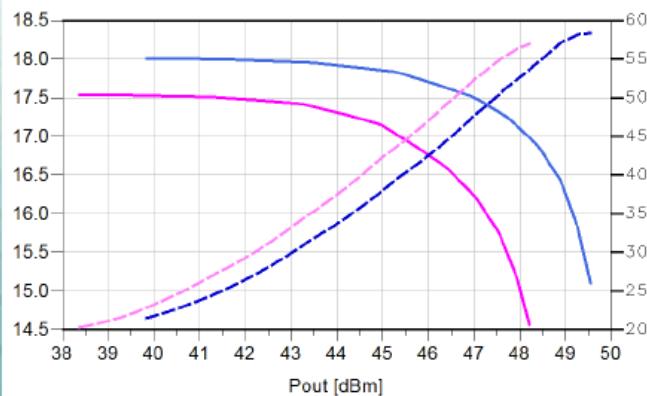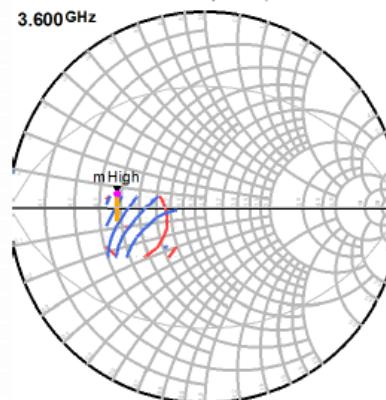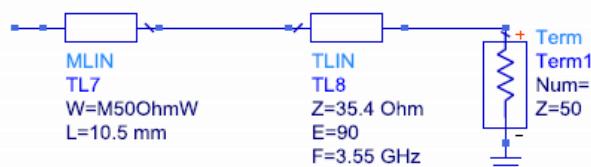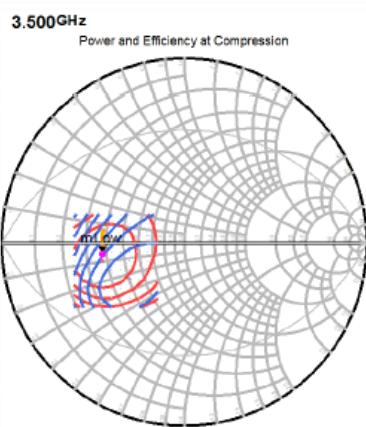

	3.500GHz	3.600GHz
Pout	49.54dBm	48.20dBm
Pout	89.92W	66.11W
Eff	58.37%	56.96%



**Any Questions?  
Thanks**



# Reference:

- [1] J. Qureshi, N. Li, W. Neo, F. van Rijs, I. Blednov, and L.de Vreede, "A Wide-Band 20W LMOS Doherty Power Amplifier," in 2010 IEEE MTT-S Int. Microwave Symp. Dig., may 2010, pp. 1504-1507.
- [2] Charles F. Campbell, "A fully integrated Ku-band Doherty amplifier MMIC," in IEEE microwave and guided wave letters, Vol. 9, No. 3, March 1999
- [3] Masaya Iwamoto, Aracely Williams, Pin-fan Chen, Andre G. Metzger, Lawrence E. Larson, Peter M. Asbeck, "An extended Doherty amplifier with high efficiency over a wide power range", IEEE transactions on microwave theory and techniques, Vol. 49, No. 12, Dec. 2001
- [4] Daehyun Kang, Dongsu Kim, Yunsung Chao, Byungjoon park, Jooseung Kim, Bumman Kim, "Design of bandwidth-enhanced Doherty power amplifier for handset applications", IEEE transactions on microwave theory and techniques, Vol.59, No.12, Dec. 2011
- [5] Bumman Kim, Ilju Kim, Junghwan Moon, "Advanced Doherty architecture", IEEE microwave magazine, Aug. 2010, pp.72-86
- [6] W.H. Doherty, "A New High Efficiency Power Amplifier for Modulated Waves", *Proc. IRE*, vol. 24, pp. 1163-1182, Sept. 1936.
- [7] N. Srirattana, et. al., "Analysis and Design of a High-Efficiency Multistage Doherty Power Amplifier for Wireless Communications", *IEEE trans. on MTT*, vol. 53, No. 3, March 2005, page 852-860
- [8] W.C.E Neo, et.al., "A Mixed-signal Approach Towards Linear and Efficient N-way Doherty Amplifiers", *IEEE trans. on MTT*, vol. 55, No. 5, May 2007, page 866-879
- [9] D. Gustafsson, J. Chani, D. Kyulenstierna, I. Angelov, N. Rorsman, and C. Fager, "A Wideband and Compact GaN MMIC Doherty Amplifier for Microwave Link Applications," submitted to *IEEE Transactions on Microwave Theory and Techniques*, May 2012
- [10] Gajadharsing, J. R., "Analysis and design of a 200W LDMOS based Doherty amplifier for 3G base stations," IEEE MTT-S International Microwave Symposium Digest, Vol. 2, 529–532, 2004
- [11] Marco J. Pelk, W.C. Edmund Neo, John R. Gajadharsing, Raymond S. Pengelly, Leo C.N. de Vreede, " A high-Efficiency 100-W GaN Three-Way Doherty Amplifier for Base-Station Applications", IEEE transactions on microwave theory and techniques, June, 2008